
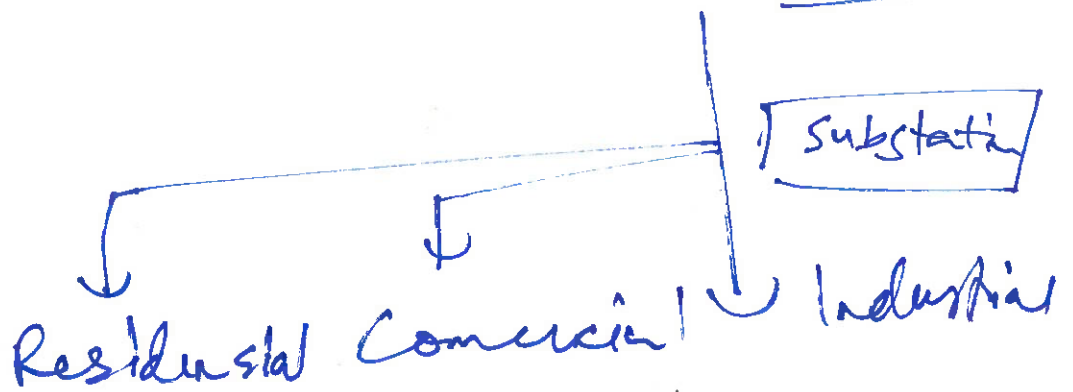


①



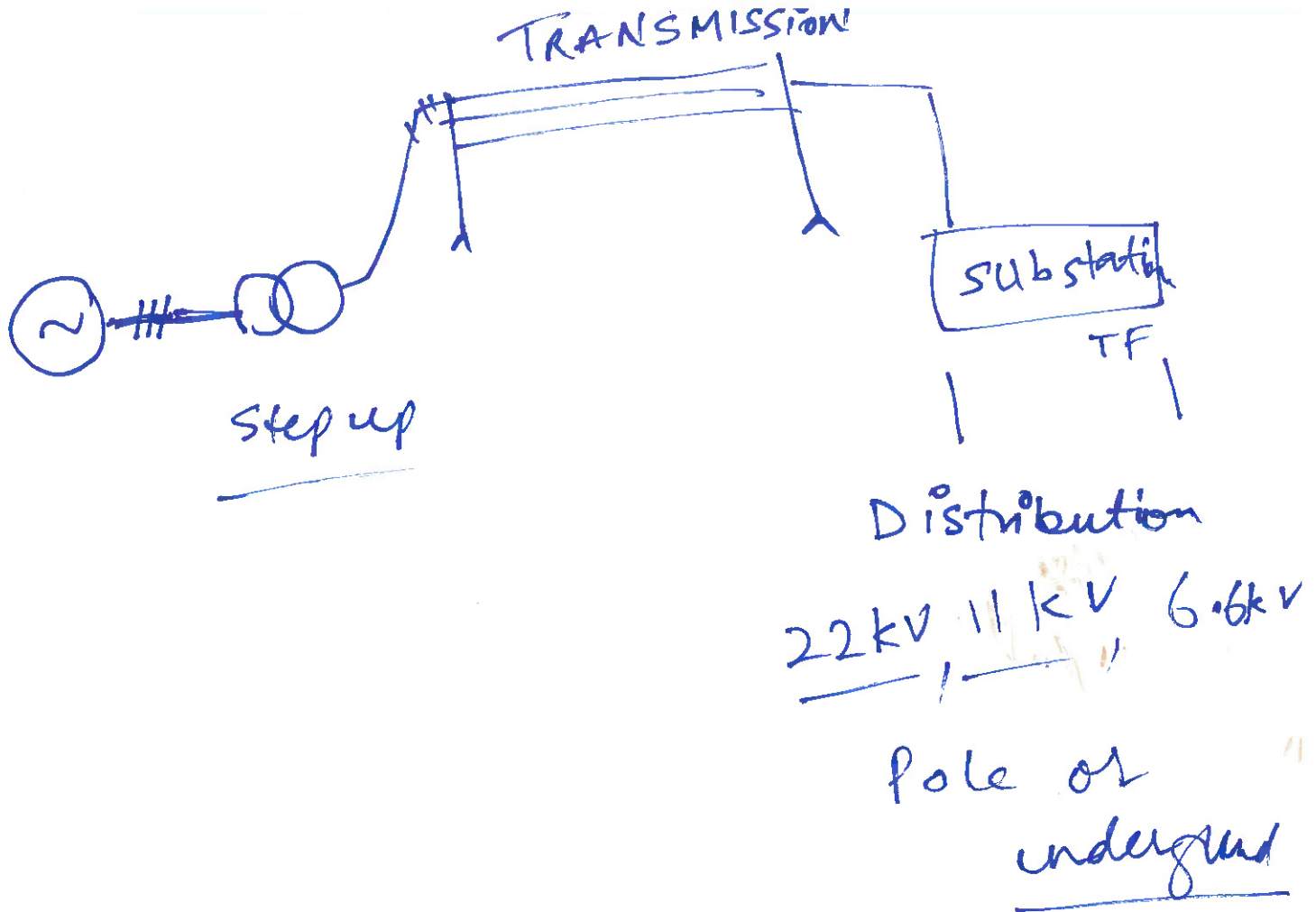


V_L — $V_{LL} = 400 \text{ kv}$ 3 ϕ

$V_p = \frac{400 \text{ kv}}{\sqrt{3}}$

(2)

Star OR delta

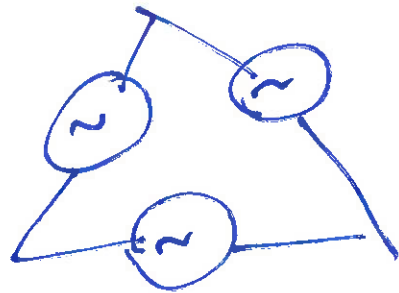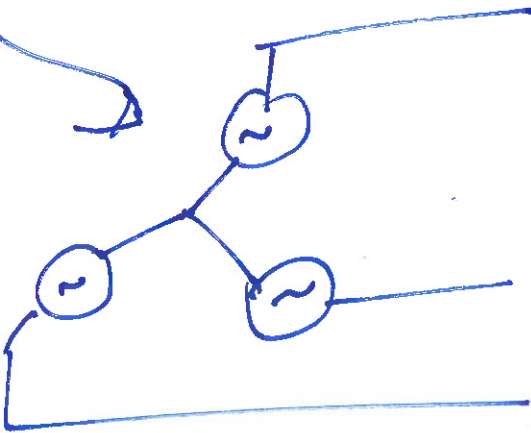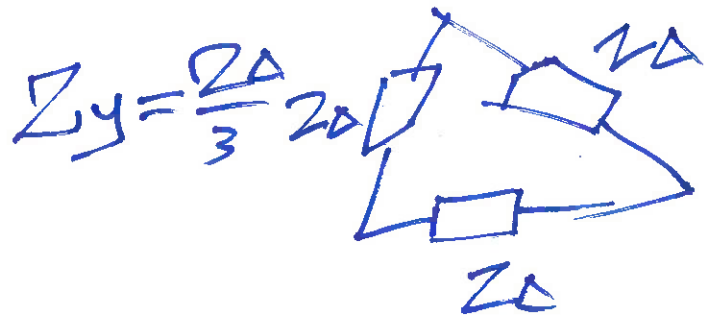


③

$$S = 1000 \text{ kVA}$$

$$V = 11 \text{ kV}$$

$$L = 5 \text{ mH}$$

$$R = 0.1 \Omega$$

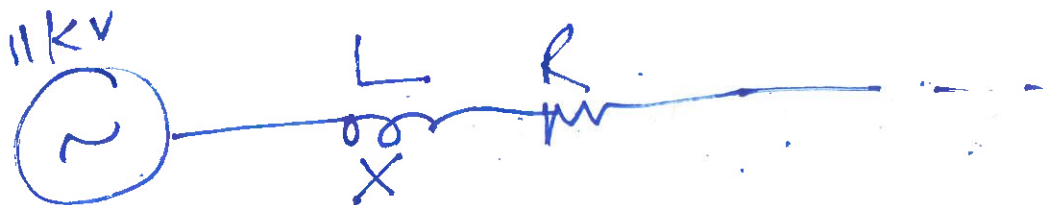

$$Z_{\text{base}} = \frac{V_n^2}{S}$$

$$R_{\text{pu}} = \frac{R}{Z_{\text{base}}}$$


$$X_{\text{pu}} = \frac{2\pi f L}{Z_{\text{base}}}$$

$$S_{\text{pu}} = \frac{S}{S_n}$$

$$V_{\text{pu}} = \frac{11 \text{ kV}}{11 \text{ kV}} = 1$$

④

PF - PROBLEM

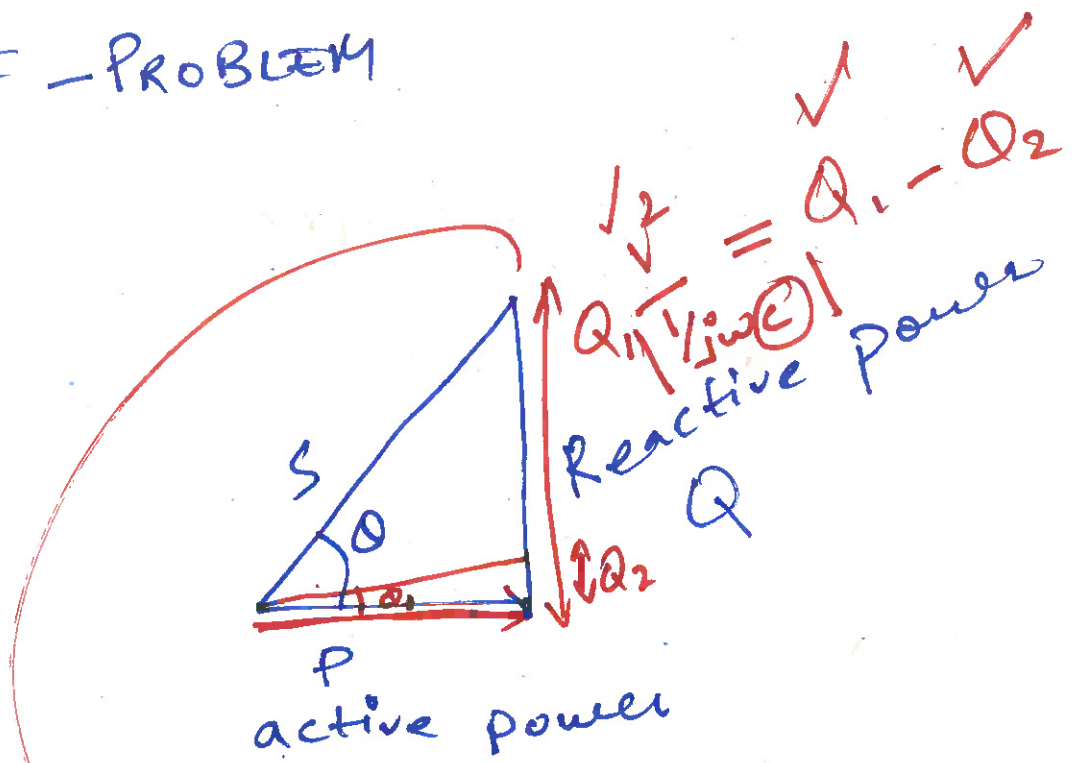


$$PF = \cos \theta \approx 1$$

$$\underline{V^2 \omega C} = Q_1 - Q_2$$

$$C = \frac{Q_1 - Q_2}{V^2 \omega}$$

IF $V = \sin \theta$

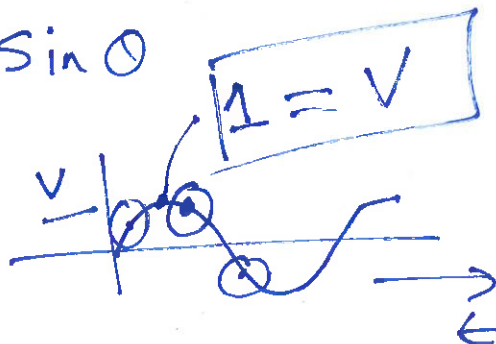

⑤

$$3\phi = 35.4 \text{ kV}$$

$$V_{ph} = \frac{35.4 \text{ kV}}{\sqrt{3}} \quad V_{rms}$$



$$V_{ph-pk} = \frac{35.4 \text{ kV} \sqrt{2}}{\sqrt{3}}$$

OR

$$= \frac{35.4 \text{ kV}}{\sqrt{\frac{3}{2}}}$$

(6)

$$X_{pu} = 2$$

$$R_{pu} = 0.5$$

$$V = 13.8 \text{ kV} \xrightarrow{10 \text{ MVA}} \text{sys voltage}$$

$$C = 1 \text{ MVA}$$

$$13.8 \text{ kV}$$

$$X_{pu} = \frac{X}{Z_{base}}$$

$$R_{pu} = \frac{R}{Z_{base}}$$

$$X_c = \frac{V^2}{S}$$

$$Z_{base} = \frac{(13.8 \text{ k})^2}{10 \text{ MVA}} = 19.4 \Omega$$

$$X_{pu} * Z_{base} = X$$

$$2 * 19.4 = X$$

$$X = 2\pi f L$$

$$R = R_{pu} * Z_{base}$$

$$R = 0.5 * 19.4 \Omega$$

(7)

$$X_C = \frac{v^2}{s} = \frac{(13.8 \text{ k})^2}{1 \text{ M}}$$

$$X_C = ?$$

$$X_C^v = \frac{1}{2\pi f C^v}?$$

FROM SLIDE 15 $t' \approx 3.3 \checkmark$

$$t = t' * T$$



$$\textcircled{t} = \textcircled{t'} * \sqrt{\frac{L}{C}} \checkmark$$

Sag Caused by Starting of Induction Motor

- Using voltage divider, standing voltage V_{sag} at the node of motor starting

$$V_{sag} = \frac{Z_{motor}}{Z_{motor} + Z_{sys}}$$

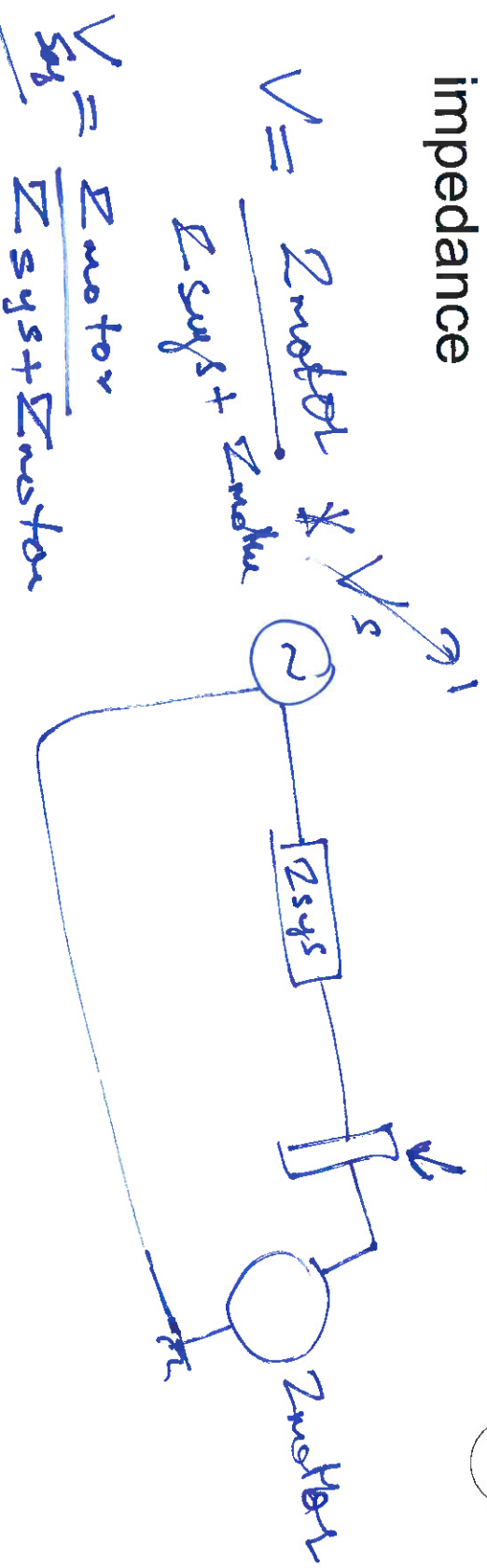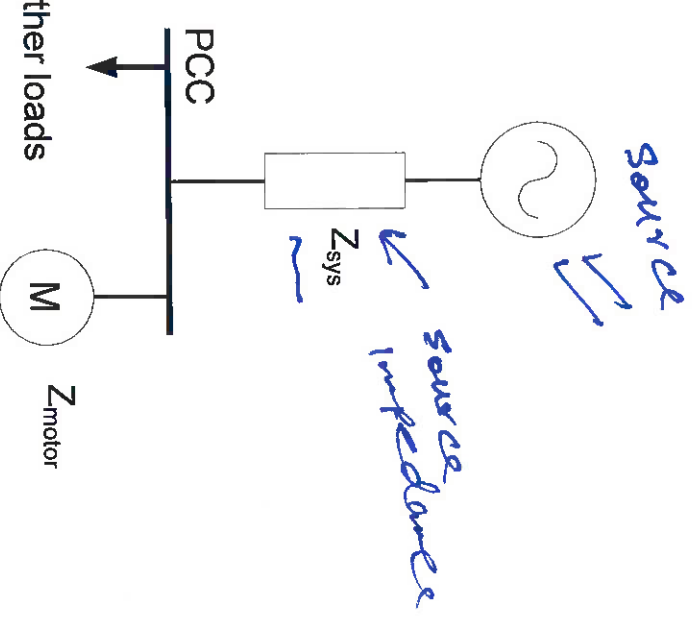- Assuming source voltage of 1.0 p.u.,
- At starting, Z_{motor} is locked-rotor impedance



Sag Caused by Starting of Induction Motor


- When starting a motor from source with a short circuit capacity S_{source} .

$$\underbrace{Z_{sys}} = \frac{V_n^2}{\underbrace{S_{source}}} ; Z_{motor} = \frac{V_n^2}{\underbrace{\beta S_{motor}}}$$

- ✓ V_n is rated voltage

- ✓ β is the ratio between the motor's starting current and the nominal current
i.e. ratio of locked-rotor current at rated voltage to rated current

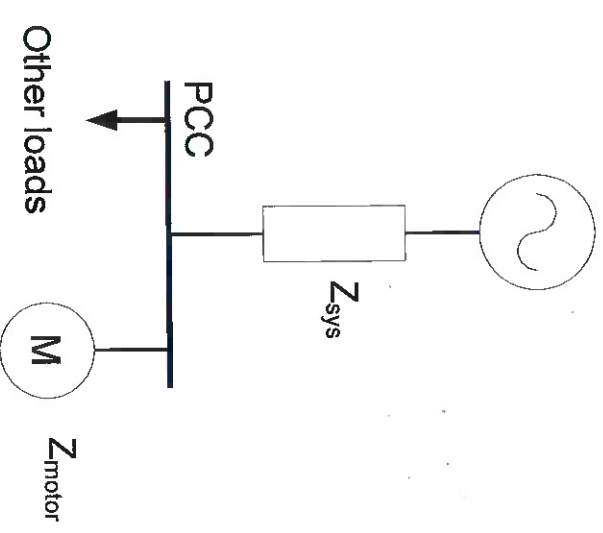- ✓ S_{motor} is the motor rated apparent power



Sag Caused by Starting of Induction Motor

$$V_{sag} = \frac{Z_{motor}}{Z_{motor} + Z_{sys}} \quad \checkmark$$

$$V_{sag} = \frac{\frac{\beta S_{motor}}{V_n^2}}{\frac{\beta S_{motor}}{V_n^2} + \frac{1}{S_{source}}} \quad \checkmark$$

$$V_{sag} = \frac{\frac{\beta S_{motor}}{1}}{\beta S_{motor} S_{source} + S_{source}}$$

$$V_{sag} = \frac{S_{source}}{S_{source} + \beta S_{motor}} \quad \checkmark \checkmark$$

- The corresponding per-unit change in voltage or voltage sag,


$$\Delta V = 1 - V_{sag} = 1 - \frac{S_{source}}{S_{source} + \beta S_{motor}}$$

$$\Delta V \approx \frac{\beta S_{motor}}{S_{source}}$$

for $S_{source} \gg \beta S_{motor}$

$$= \frac{\beta S_{motor}}{S_{source} + \beta S_{motor}} \quad \checkmark$$

$S_{source} + \beta S_{motor}$

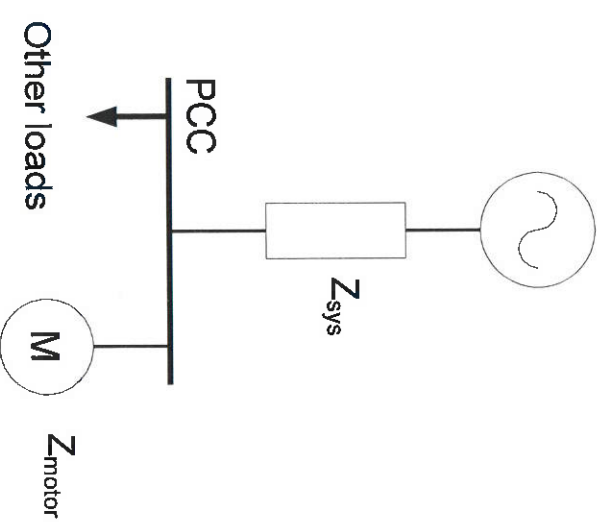

$S_{source} + \beta S_{motor}$

Motor-Starting Methods

$$P_s = \frac{V_p^2}{0.2 \pi n} \alpha$$

- Autotransformer with turn ratio $\alpha = N_2 / N_1$

$$V_{start} = V_{sec} = \frac{N_2}{N_1} V_{pri} = \alpha V_{pri}$$


$$\Rightarrow I_{start-sec} = \frac{V_{sec}}{Z_{motor}} = \frac{\alpha V_{pri}}{Z_{motor}}$$

$$I_{start-sec} = \alpha I_{start-original}$$

$$I_{start-pri} = \alpha I_{start-sec}$$

$$\therefore I_{start-pri} = \alpha^2 I_{start-original}$$
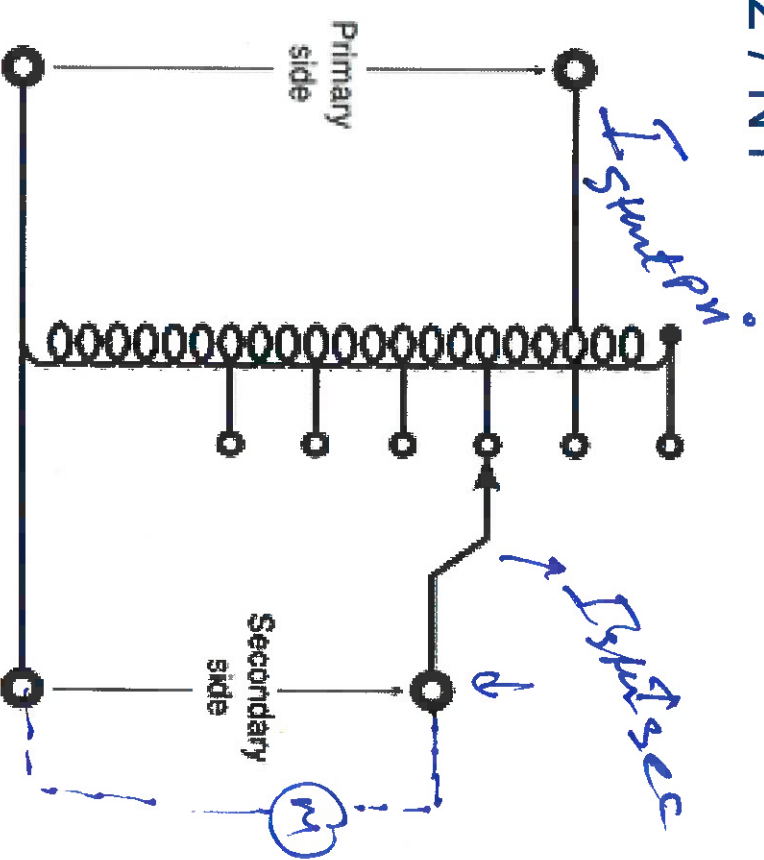
$$\Rightarrow \beta_{autotransformer} = \alpha^2 \times \beta_{original}$$



$$\beta = \frac{I_{start}}{I_{running}}$$