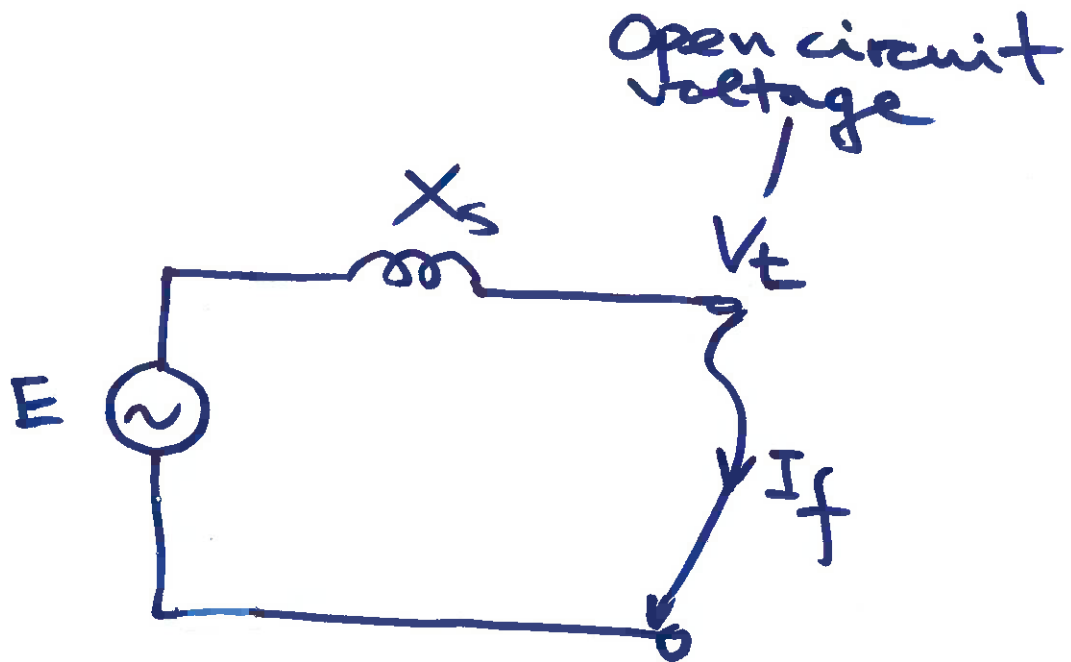


- Not all generated harmonic current flows through the harmonic filter
 - Some is absorbed by parallel load and some will go into the utility source
 - Worst case (highest current through filter) is with negligible parallel load and a high impedance (low fault current) source

Fundamental		Harmonic order			
System		5th	7th	11th	13th
System voltage	34.5				
Short circuit current	10				
Impedance	1.992				
X/R ratio	10				
System reactance	1.982				
System resistance	0.198				
<i>S = 53 MVA</i>					
Filter					
Size	7420	rated kvar			
Current	124.2	Amperes			
Impedance	160.4	Ohms	4.4	29.2	68.4
Tuning	4.7	Harmonic order			
Capacitive reactance	168.0	Ohms		24.0	15.3
Inductive reactance	7.6	Ohms		53.2	83.7
<i>S = 53 MVA</i>					
Rectified load					
Total including factor of safety	30000	kva			
Current	502.0	Amperes	71.7	45.6	38.6
<i>$\frac{502}{5} \rightarrow 100.4$</i>					
System					
Parallel impedance		Ohms	9.45	16.61	19.92
Voltage (line to ground)	19918.6	Volts	677.9	758.1	769.2
<i>$100.4 \rightarrow 308.0$</i>					
Filter Harmonic current	1311.7	Amperes	23.2	11.1	8.9
<i>$\frac{1311.7}{4.4} \rightarrow 300.4$</i>					
Total harmonic voltage	1311.7	Volts (rms)			
Voltage THD	6.59	Percent			
<i>$\frac{308}{4.4} \rightarrow 70.0$</i>					
		<i>$= \sqrt{308^2 + 677.9^2 + 758.1^2 + 769.2^2}$</i>			



$$I_f = \frac{E}{X_s}$$

Before the fault

$$E = V_t$$

$$\therefore I_f = \frac{V_t}{X_s}$$

$$\Rightarrow X_s = \frac{V_t}{I_f} = \frac{34.5/\sqrt{3} \text{ kV}}{10 \text{ kA}} = 1.992 \Omega$$

$$Z_s = \frac{34.5 \text{ kV}/\sqrt{3}}{10 \text{ kA}}$$

$$= 1.992 \Omega$$

$$Z_s = \sqrt{R_s^2 + X_s^2}$$

$$= \sqrt{0.198^2 + 1.982^2}$$

$$= 1.992 \Omega$$

where R_s, X_s are given

$$\frac{X}{R} = \frac{1.982}{0.198} = 10$$

$$S = \sqrt{3} V_L I_L$$

$$7420 = \sqrt{3} V_L I_L$$

$$\begin{aligned}\therefore I_L &= \frac{7420}{\sqrt{3} \times 34.5} \\ &= \underline{124.2 \text{ A}}\end{aligned}$$

$$S = \sqrt{3} V_L I_L$$


$$30000 = \sqrt{3} \times 34.5 \times I_L$$

$$\begin{aligned}\therefore I_L &= \frac{30000}{\sqrt{3} \times 34.5} \\ &= \underline{502.4 \text{ A}}\end{aligned}$$

At $f_r = 300 \text{ Hz}$, $X_C = X_L$

At 6% below $f_r = 300 \text{ Hz}$

$$X_{\text{eff}} = X_C - X_L$$

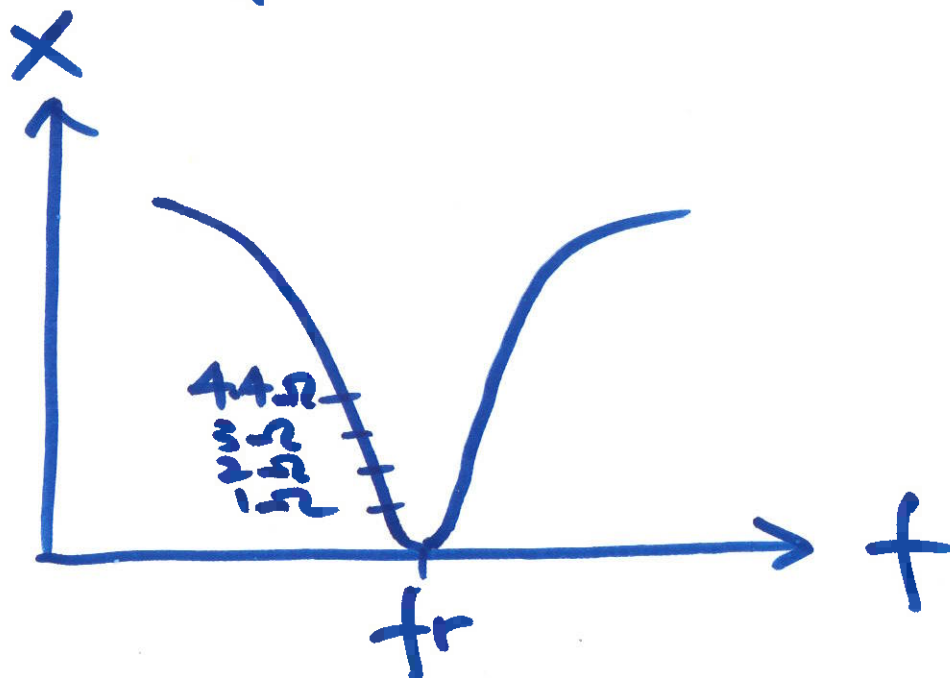

Due to system impedance variation
filter reactance variation,
component variation, etc.

$$4.4 \Omega \xrightarrow{\text{shift}} 0 \Omega$$

- Total harmonic voltage across the capacitor,
 $V_C(1) = I_f(1) X_C = 124 \times 168 = 20,832 \text{ V}$

$$V_C(h) = \sum_h I_f(h) \left(\frac{X_C}{h} \right) = 69.6 \times \frac{168}{5} + 23.2 \times \frac{168}{7} + 11.1 \times \frac{168}{11} + 8.9 \times \frac{168}{13} = 3,180 \text{ V}$$

- Voltage rating of the capacitor,
 $V_r = V_C(1) + V_C(h) = 20,832 + 3,180 = 24,012 \text{ V}$
- Design should rate capacitor voltage at 100%, and reserving the 110% rms voltage and 120% peak voltage margins for contingency operation
- Based on line-to-line rated voltage and its impedance, the rated three-phase MVAR of the capacitor bank,

$$Q_{\text{rated}} = \frac{(\sqrt{3}V_r)^2}{X_C} = \frac{(\sqrt{3} \times 24,012)^2}{168.4} = 10.27 \text{ MVAR}$$

- Capacitor rated MVAR is significantly larger than the filter effective reactive power (7.4 MVAR) because capacitor voltage rating is higher than nominal system voltage
- Nominal capacitor current based on rated voltage and MVAR,

$$I_{\text{nom}} = \frac{Q_{\text{rated}}}{\sqrt{3}V_{\text{rated}}} = \frac{10.27 \text{ MVAR}}{\sqrt{3} \times (\sqrt{3} \times 24 \text{ kV})} = 142.6 \text{ A}$$

$$\frac{144.8}{142.6} = 101.5\%$$

The calculated filter current of 144.8 A is only 101.5% of this nominal current, and thus complying with IEEE Std 18 (<135%)

- Dielectric heating of the capacitor must be acceptable,

$$\left| \sum_h (V(h) I(h)) \right| \leq |1.35 Q_{\text{rated}}|$$

$69.6 \times \frac{168}{5} / 23.2 \times \frac{168}{5}$

$$|3 \times (20.83 \times 124 + 2.34 \times 69.6 + 0.56 \times 23.2 + 0.17 \times 11.1 + 0.12 \times 8.9)| \leq |1.35 \times 10270|$$

$$8,285 \leq 13,865$$

- Filter capacitor is conservatively designed and meets all requirements
- Good to build certain contingency for harmonics from unidentified sources or new non-linear loads

- Filter reactor can be located at the source side of the capacitor or the neutral side
- If located at the source side, it should be rated to withstand a short circuit to ground at the junction between reactor and capacitor,


$$X_s = \frac{V_{\text{ll,nom}}}{\sqrt{3} I_{\text{SCBUS}}} = \frac{34.5 \text{ kV}}{\sqrt{3} \times 10 \text{ kA}} = 1.99 \Omega$$

$$I_{\text{SC}} = \frac{V_{\text{ll,nom}}}{\sqrt{3} (X_s + X_L)} = \frac{34.5 \text{ kV}}{\sqrt{3} \times (1.99 + 7.63)} = 2.07 \text{ kA}$$

- $V_{\text{ll,nom}}$ nominal system line-to-line voltage
- I_{SCBUS} available short-circuit current at bus
- I_{SC} symmetrical short-circuit rating of reactor

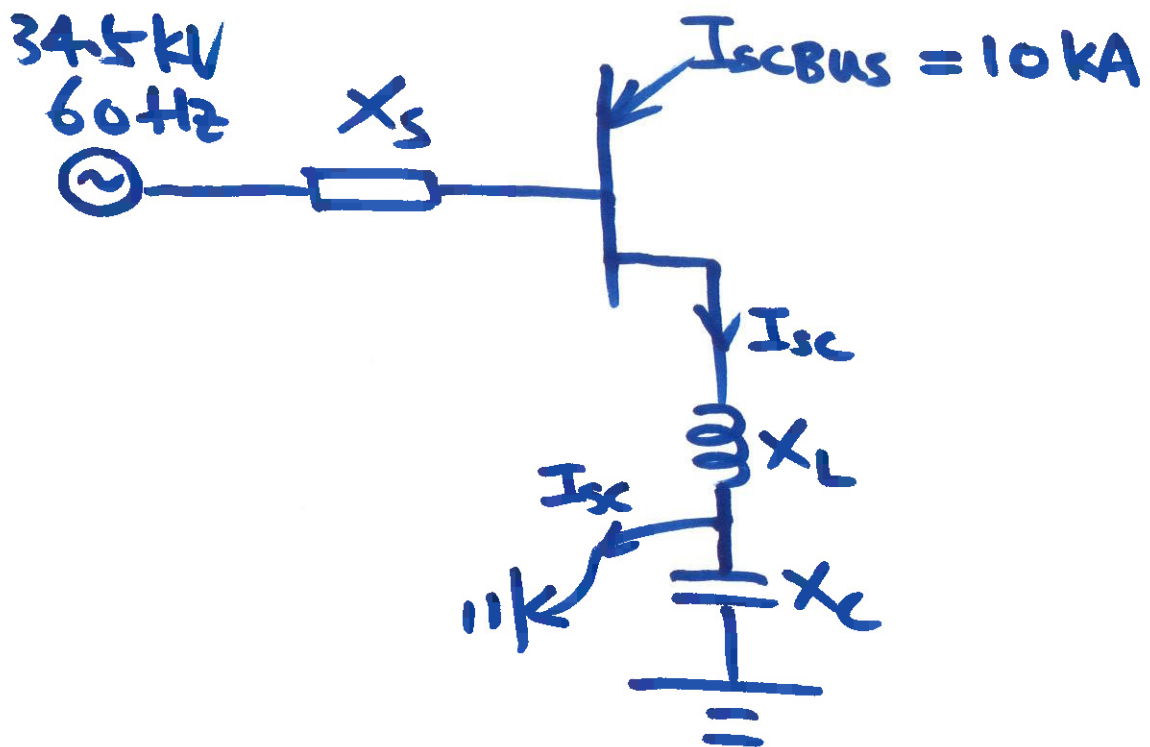- The quality factor Q (X/R ratio) of harmonic filter is not critical in most application, but is usually above 50






$$X_s = \frac{V_L / \sqrt{3} \text{ kV}}{I_{scBus} \text{ kA}} \Omega$$

$$I_{sc} = \frac{V_L / \sqrt{3} \text{ kV}}{(X_s + X_L)} \text{ kA}$$

(19)

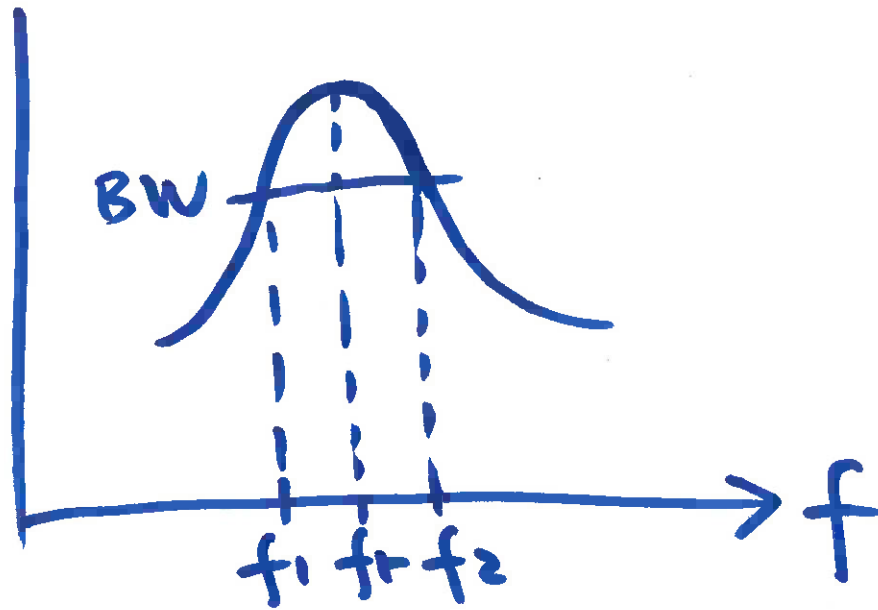

$Q > 50$, more selective

high Q affects the filter
"selectivity" which means
more selective.


$$BW = \frac{f_r}{Q} \Rightarrow Q \uparrow = \frac{f_r}{BW \downarrow}$$

The smaller the BW,
the higher the circuit
selectivity.

(1) 12-pulse system
 $12k \pm 1$

(2) 24-pulse system
 $24k \pm 1$

At PCC, voltage distortion

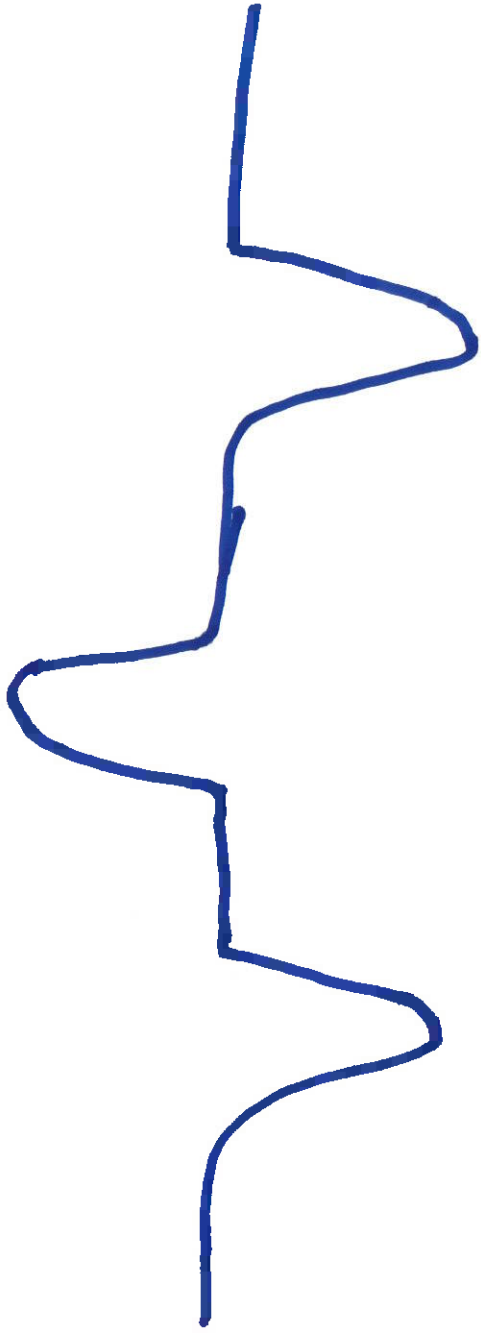


$$\textcircled{1} \quad \downarrow S_{CR} = \frac{I_{sc}}{I_L \uparrow}$$

$$\textcircled{2} \quad \uparrow S_{CR} = \frac{I_{sc}}{I_L \downarrow}$$

$$\textcircled{3} \quad \downarrow S_{CR} = \frac{I_{sc} \downarrow}{I_L}$$

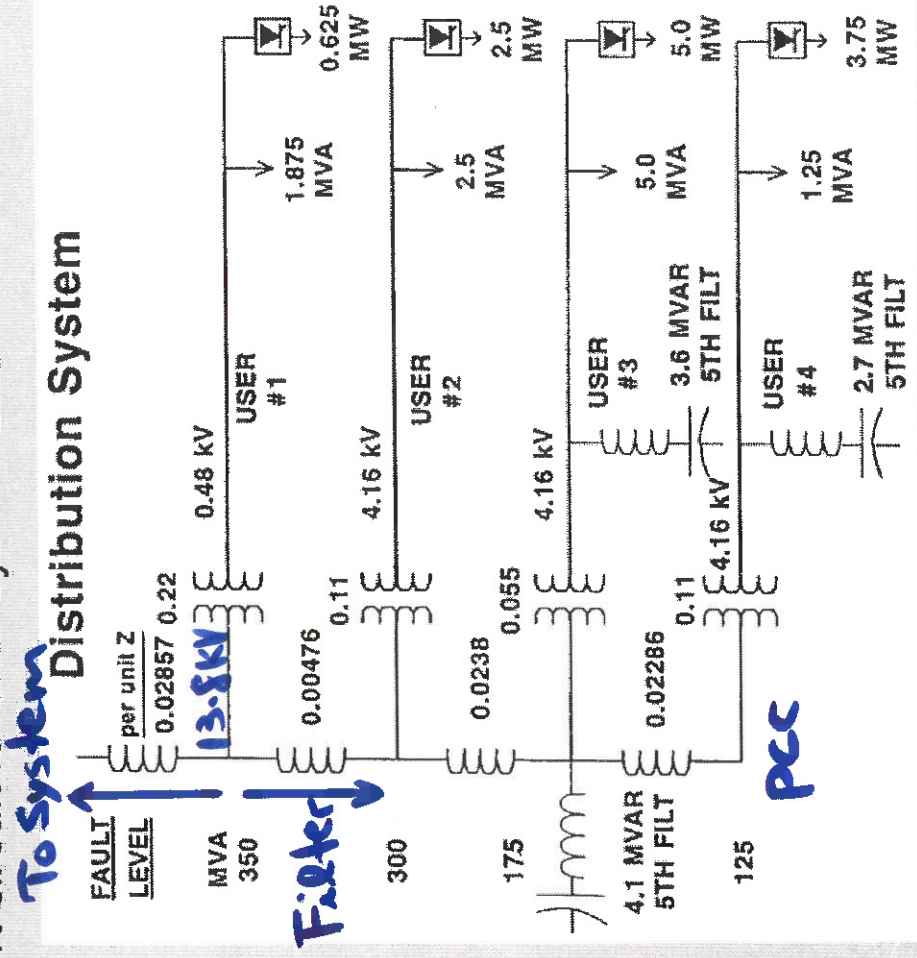Example of meeting harmonic limits

- A utility distribution feeder with four users along the feeder
 - Evaluate if meeting limit requirements and effectiveness of harmonic filter
 - Each user sees a different short circuit level or system size
 - User 1 @ I_{sc} / I_L ratio of 140
 - 350MVA, 14.6kA system
 - 2.5MVA, 104A load
 - 25% is converter with 26A
 - User 2 @ I_{sc} / I_L ratio of 60
 - 300MVA, 12.55kA system
 - 5MVA, 209A load
 - 50% is converter with 105A
 - User 3 @ I_{sc} / I_L ratio of 17.5
 - 175MVA, 7.32kA system
 - 10MVA, 418A load
 - 50% is converter with 209A
 - User 4 @ I_{sc} / I_L ratio of 25
 - 125MVA, 5.2kA system
 - 5MVA, 209A load
 - 75% is converter with 157A



User #1

$$I_{sc} = \frac{350 \text{ MVA}}{\sqrt{3} \times 13.8 \text{ kV}} = \underline{\underline{14.6 \text{ kA}}}$$

$$I_1 = \frac{2.5 \text{ MVA}}{\sqrt{3} \times 13.8 \text{ kV}} = \underline{\underline{104 \text{ A}}}$$

$$SCR = \frac{I_{sc}}{I_1} = \underline{\underline{140}}$$

$$25\% \times 104 \text{ A} = \underline{\underline{26 \text{ A}}}$$

$$\text{Converter Load} = \frac{0.625}{2.5}$$

$$= 0.25 \text{ or } 25\%$$

User #1

Harmonic Currents (Amperes)

	5	7	11	13	17	19	23	25	29	31	35	THD
<u>Case A</u> To System	4.99 104	3.43	1.90	1.48	0.91	0.70	0.52	0.42	0.36	0.31	0.29	
% Distortion	4.80	3.33	1.83	1.42	0.87	0.67	0.50	0.40	0.35	0.30	0.28%	6.42%
<u>Case B</u> To System	2.49 104	2.49	1.49	1.18	0.73	0.56	0.42	0.34	0.29	0.25	0.23	
To Filter	2.49	0.94	0.40	0.30	0.18	0.14	0.10	0.08	0.07	0.06	0.05	
% Distortion	2.39	2.39	1.43	1.13	0.70	0.54	0.40	0.33	0.28	0.24	0.22%	4.00%
<u>Case C</u> To System	3.50 104	2.67	1.53	1.20	0.74	0.57	0.43	0.34	0.30	0.25	0.24	
To Filter	1.48	0.76	0.37	0.28	0.17	0.13	0.09	0.08	0.06	0.06	0.05	
% Distortion	3.77	2.57	1.47	1.15	0.71	0.55	0.40	0.33	0.29	0.24	0.23%	4.76%
<u>Case D</u> To System	2.50 104	2.36	1.42	1.12	0.70	0.53	0.40	0.32	0.28	0.24	0.22	
To Filter	2.49	1.08	0.48	0.36	0.22	0.16	0.12	0.10	0.08	0.07	0.07	
% Distortion	2.40	2.26	1.36	1.07	0.67	0.51	0.38	0.31	0.27	0.23	0.21%	3.04%
IEEE Std 519 Limits	12%		5.5%		5.0%		2.0%		1.0%		15%	

User #2

Harmonic Currents (Amperes)

	5	7	11	13	17	19	23	25	29	31	35	THD
<u>Case A</u> To System	20.2	13.9	7.66	5.99	3.68	2.84	2.10	1.68	1.47	1.26	1.16	
% Distortion	9.67	6.65	3.67	2.87	1.76	1.36	1.00	0.80	0.70	0.60	0.56%	13.0%
<u>Case B</u> To System	8.42	9.44	5.76	4.56	2.84	2.20	1.63	1.31	1.14	0.98	0.90	
To Filter	11.8	4.41	1.90	1.43	0.84	0.64	0.47	0.37	0.32	0.28	0.25	
% Distortion	4.03	4.52	2.76	2.18	1.36	1.05	0.78	0.63	0.55	0.47	0.44%	7.35%
<u>Case C</u> To System	13.2	10.3	5.94	4.68	2.89	2.24	1.66	1.33	1.16	1.00	0.92	
To Filter	7.01	3.6	1.72	1.31	0.79	0.60	0.44	0.35	0.31	0.26	0.24	
% Distortion	6.32	4.93	2.84	2.24	1.38	1.07	0.79	0.64	0.56	0.48	0.45%	9.1%
<u>Case D</u> To System	8.43	8.79	5.38	4.27	2.66	2.06	1.53	1.23	1.07	0.92	0.85	
To Filter	11.8	5.07	2.28	1.72	1.02	0.78	0.57	0.45	0.39	0.34	0.31	
% Distortion	4.03	4.21	2.57	2.04	1.27	0.99	0.73	0.59	0.51	0.44	0.41%	7.0%
IEEE Std 519 Limits	10%		4.5%		4.0%		1.5%				0.7%	12%

User #3

Harmonic Currents (Amperes)

	5	7	11	13	17	19	23	25	29	31	35	THD
<u>Case A</u> To System	40.1	27.6	15.3	11.9	7.31	5.64	4.18	3.34	2.93	2.5	2.3	
% Distortion	9.59	6.60	3.66	2.85	1.75	1.35	1.00	0.80	0.70	0.60	0.55%	12.8%
<u>Case B</u> To System	0.01	12.5	8.78	7.03	4.44	3.45	2.58	2.07	1.82	1.56	1.44	
To Filter	40.1	15.1	6.52	4.87	2.87	2.19	1.60	1.27	1.11	0.94	0.86	
% Distortion	0.00	2.99	2.10	1.68	1.06	0.83	0.62	0.50	0.44	0.37	0.34%	4.37%
<u>Case C</u> To System	0.02	9.73	7.10	5.73	3.64	2.83	2.12	1.70	1.50	1.28	1.18	
To Filter	40.1	17.9	8.20	6.17	3.67	2.81	2.06	1.64	1.43	1.22	1.12	
% Distortion	0.00	2.33	1.70	1.37	0.87	0.68	0.51	0.41	0.36	0.31	0.28%	3.48%
<u>Case D</u> To System	0.04	10.3	7.50	6.05	3.84	2.99	2.24	1.80	1.58	1.35	1.25	
To Filter	40.1	17.3	7.80	5.85	3.47	2.65	1.94	1.54	1.35	1.15	1.05	
% Distortion	0.00	2.46	1.79	1.45	0.92	0.72	0.54	0.43	0.38	0.32	0.30%	3.68%
IEEE Std 519 Limits	4%		2.0%		1.5%		0.6%		0.3%		5.0%	

User #4

Harmonic Currents (Amperes)



	5	7	11	13	17	19	23	25	29	31	35	THD		
Case A To System	30.1	20.7	11.5	8.95	5.50	4.24	3.14	2.51	2.20	1.88	1.72			
% Distortion	14.4	9.90	5.50	4.28	2.63	2.03	1.50	1.20	1.05	0.90	0.82%	19.3%		
Case B To System	0.00	9.39	6.60	5.30	3.34	2.59	1.94	1.56	1.37	1.17	1.07			
To Filter	30.1	11.3	4.90	3.66	2.16	1.64	1.20	0.96	0.83	0.71	0.65			
% Distortion	0.00	4.49	3.16	2.54	1.60	1.24	0.93	0.75	0.66	0.66	0.51%	6.57%		
Case C To System	0.01	6.17	4.64	3.76	2.40	1.87	1.40	1.12	0.99	0.85	0.78			
To Filter	30.1	14.5	6.86	5.19	3.10	2.37	1.74	1.39	1.21	1.03	0.94			
% Distortion	0.00	2.95	2.22	1.81	1.14	0.89	0.67	0.54	0.47	0.41	0.37%	4.50%		
Case D To System	0.03	7.72	5.64	4.55	2.89	2.25	1.68	1.35	1.19	1.02	0.93			
To Filter	30.1	13.0	5.86	4.40	2.61	1.99	1.46	1.16	1.01	0.86	0.79			
% Distortion	0.01	3.69	2.70	2.18	1.38	1.08	0.80	0.65	0.57	0.49	0.45%	5.53%		
IEEE Std 519 Limits	7%			3.5%			2.5%			1.0%			0.5%	8.0%


Meeting harmonic voltage limits


User	Case	V ₅	V ₇	V ₁₁	V ₁₃	V ₁₇	V ₁₉	V ₂₃	V ₂₅	V ₂₉	V ₃₁	V ₃₅	THD
#1	A	3.26	3.14	2.73	2.51	2.02	1.74	1.56	1.36	1.38	1.26	1.31	7.13
	B	0.37	1.62	1.70	1.60	1.32	1.14	1.03	0.90	0.92	0.84	0.87	3.93
	C	0.57	1.18	1.24	1.18	0.97	0.85	0.77	0.67	0.68	0.62	0.65	2.94
	D	0.38	1.39	1.50	1.42	1.17	1.02	0.92	0.80	0.82	0.75	0.78	3.46
#2	A	3.77	3.63	3.16	2.91	2.34	2.02	1.81	1.57	1.60	1.46	1.51	8.25
	B	0.41	1.86	1.96	1.85	1.52	1.32	1.19	1.04	1.06	0.97	1.01	4.53
	C	0.64	1.34	1.43	1.35	1.12	0.97	0.88	0.77	0.78	0.72	0.75	3.37
	D	0.41	1.60	1.72	1.63	1.35	1.17	1.06	0.92	0.94	0.86	0.90	3.99
#3	A	5.77	5.55	4.84	4.45	3.58	3.08	2.77	2.40	2.44	2.23	2.31	12.62
	B	0.00	2.52	2.78	2.63	2.18	1.89	1.71	1.49	1.52	1.39	1.44	6.39
	C	0.39	1.64	1.87	1.78	1.49	1.29	1.17	1.03	1.05	0.96	1.00	4.34
	D	0.00	2.07	2.37	2.26	1.88	1.64	1.48	1.29	1.32	1.21	1.26	5.47
#4	A	6.59	6.35	5.53	5.09	4.09	3.52	3.16	2.75	2.79	2.55	2.64	14.43
	B	0.82	3.31	3.47	3.27	2.69	2.33	2.10	1.03	1.87	1.71	1.77	8.02
	C	0.33	1.73	2.02	1.94	1.62	1.41	1.28	1.12	1.14	1.04	1.09	4.69
	D	0.83	2.86	3.07	2.90	2.39	2.08	1.88	1.64	1.67	1.53	1.59	7.12

A = System with no filters
 B = System with 4.1 Mvar fifth harmonic filter at User #3, 13.8 kV bus
 C = System with fifth harmonic filter at User #3 and #4, 4.16 kV bus
 D = System with 5.8 Mvar fifth harmonic filter at User #3, 13.8 kV bus

Note: All values are in percent

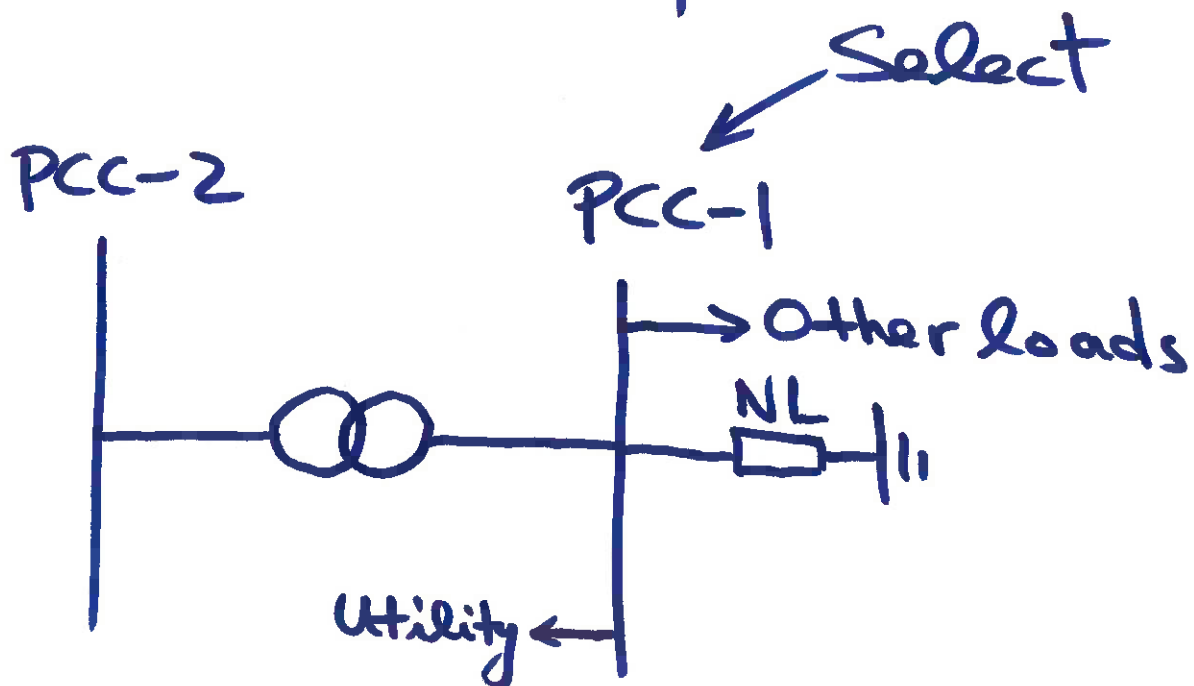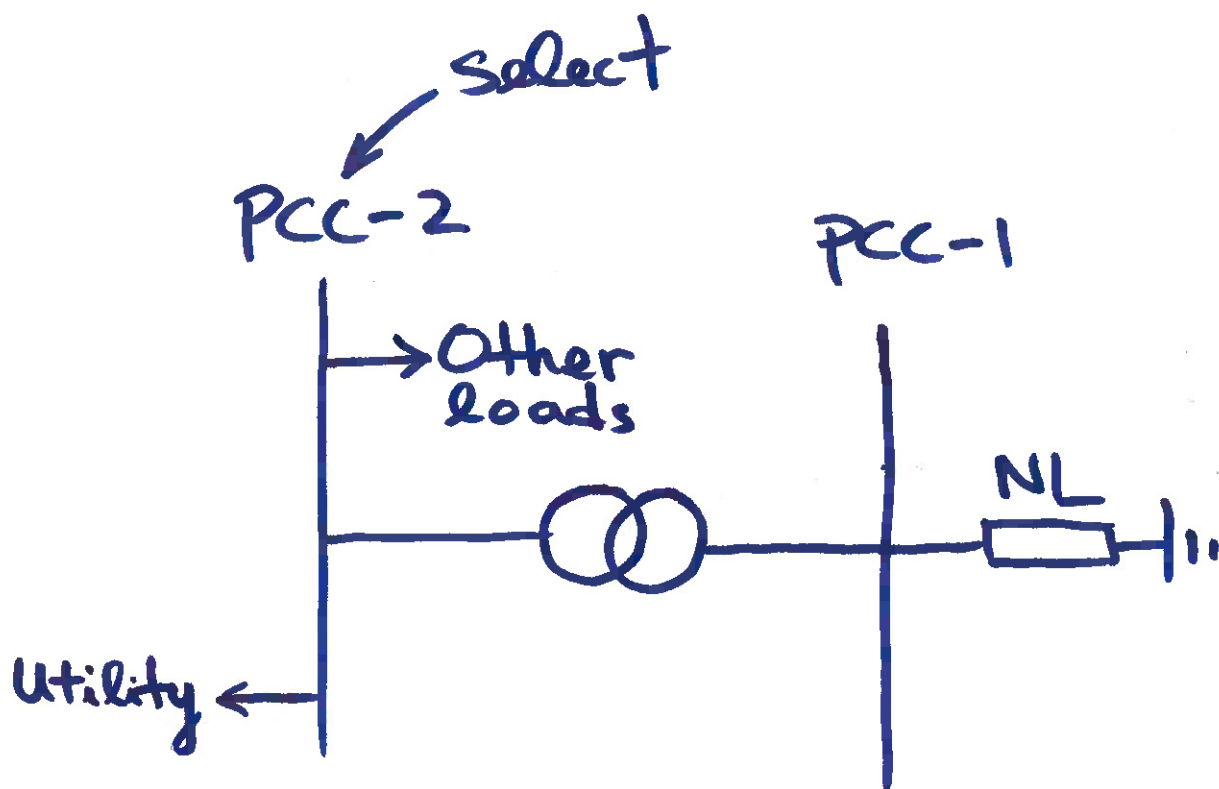

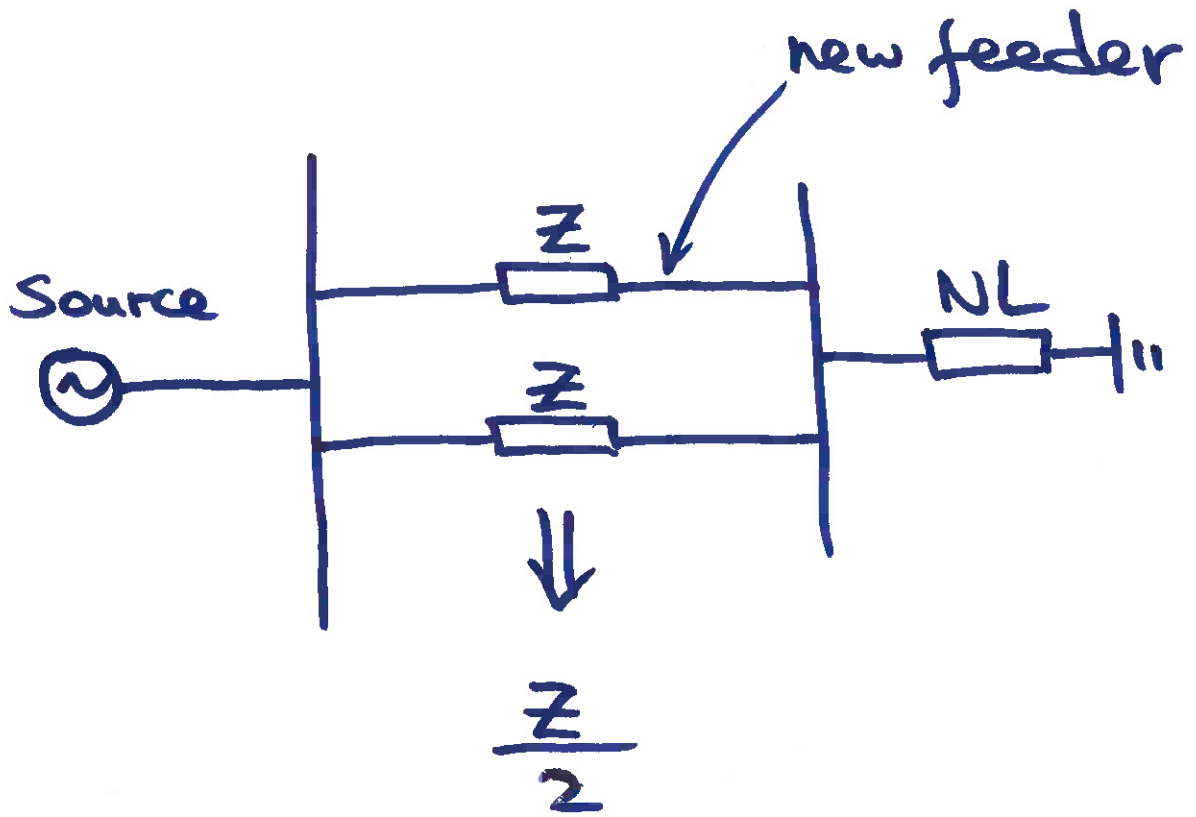

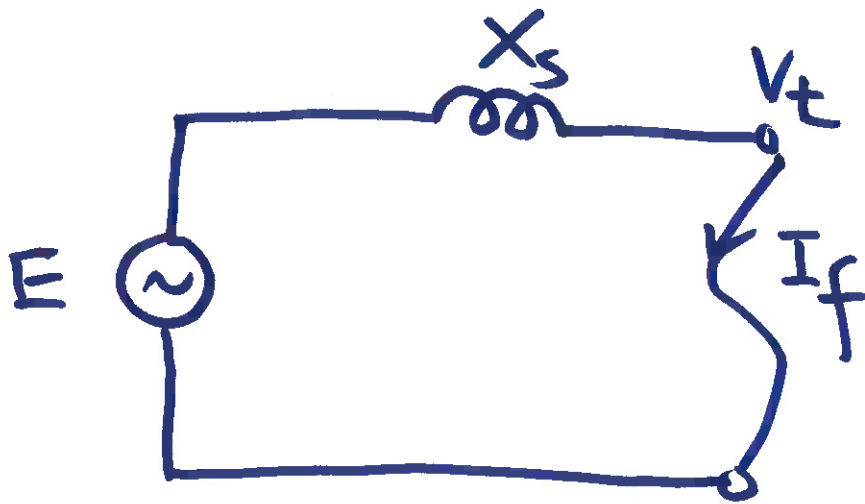

$$I_{fpu} = \frac{E_{pu}}{X_{spu}} \quad 1 \text{ pu}$$

$$I_{fpu} = \frac{1}{X_{spu}} \text{ pu}$$

$$I_{\text{actual}} = \frac{1}{X_{spu}} \times I_b \text{ A}$$

$$I_b = I_{\text{rated}}$$