

EE3010 – Electrical Devices and Machines

Semester 2, 2018-2019

Lecture Notes on

Transformers

Dr. So Ping Lam

Associate Professor

Division of Power Engineering

School of Electrical and Electronic Engineering

Nanyang Technological University

Phone: 6790 5026


Office: S1-B1c-77

Email: eplso@ntu.edu.sg

INTRODUCTION

- A simplest transformer consists of two coils wound on a common magnetic core:

- Primary Winding
- Secondary Winding

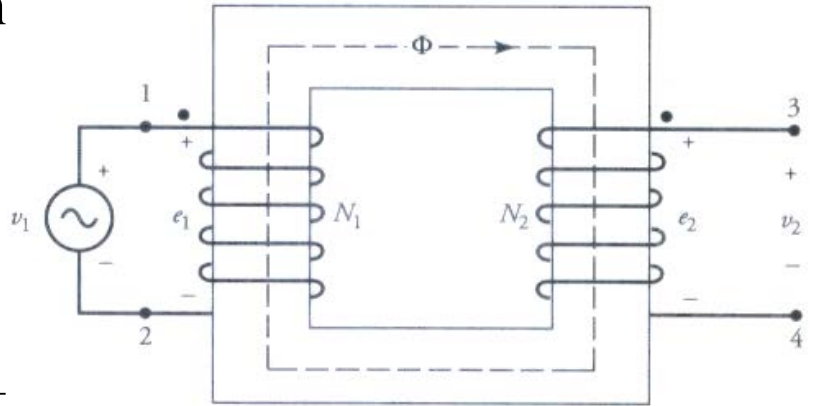

- A time varying current produced by a time varying voltage connected one winding establishes a time varying flux in the coil. The flux links the secondary winding inducing a voltage in the secondary winding.

- Step-up transformer, e.g. 110 Vac \Rightarrow 220 Vac
- Step-down transformer, e.g. 220 Vac \Rightarrow 110 Vac


Either winding can be connected to the source or the load.

- Power transfer from one winding to the secondary winding occurs through the magnetic field/magnetic flux in the core.
- The frequency in the secondary winding is the same as in the primary winding, i.e. $f_1 = f_2$.


CONSTRUCTION

- The core is made of thin ‘electrical steel’ laminations in order to reduce the core (eddy current and hysteresis) losses. The core is of two types:

(a) Shell type

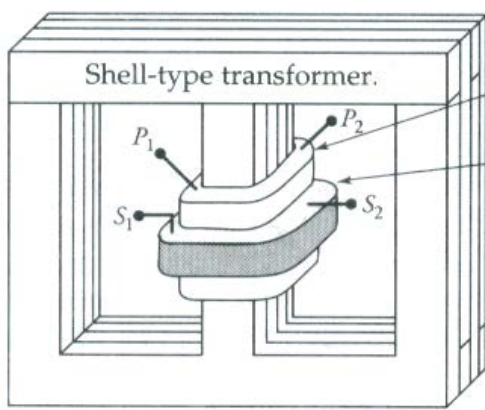

(b) Core type

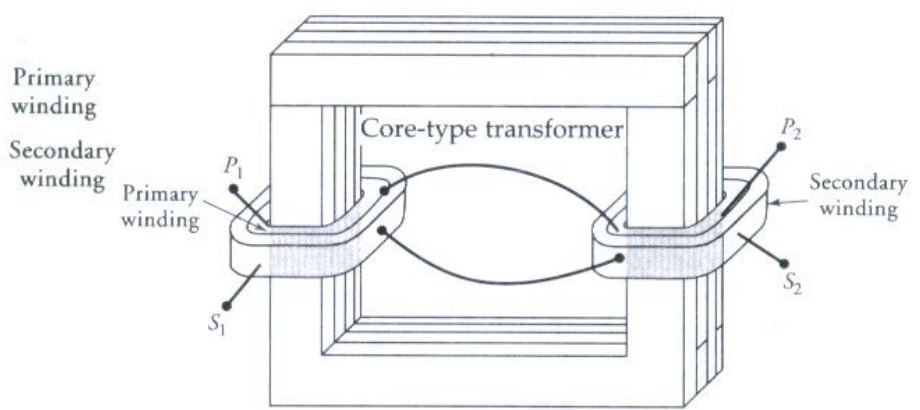

- The windings may be directly wound on the core in small transformers. However, for high-power transformers, the windings are usually form-wound and then assembled over the core.
- A cooling system is an integral part of the transformer. Usually a transformer may be cooled by natural air or forced air circulation. When natural air or forced air circulation is not enough, the whole transformer is immersed in a transformer oil tank.

IDEAL TRANSFORMER

□ The ideal condition assumptions are:

- The windings have negligible resistance \Rightarrow no copper losses in the windings, no voltage drops.
- All the flux is confined the core and therefore the same flux links both the windings. As $\mu_c \rightarrow \infty$, $R_c = (l/\mu_c A) \rightarrow 0$
- The permeability of the core is infinitely high, which implies that a vanishingly small mmf (current) is required to set up the flux ϕ . $Ni \downarrow = \phi R_c \downarrow$
- The core does not incur any hysteresis or eddy current loss \Rightarrow no core losses.


□ If the number of turns in the two windings be N_1 and N_2 , then Faraday's Law gives

$$v_1 = e_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = e_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{N_1}{N_2} = a \text{ (say)}$$

where ' a ' is called the turns ratio.

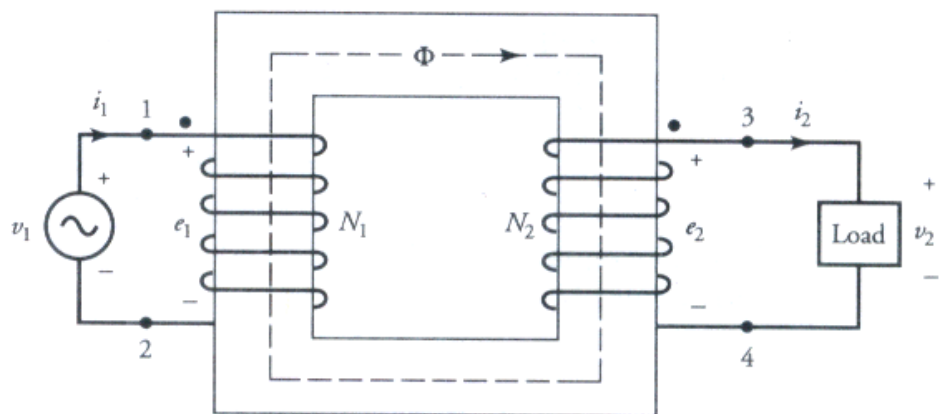

IDEAL TRANSFORMER (CONT'D)

- As the core material is ideal, the total mmf required to create the flux would be vanishingly small, so that

$$N_1 i_1 - N_2 i_2 = 0 \Rightarrow N_1 i_1 = N_2 i_2 \Rightarrow \frac{i_2}{i_1} = \frac{N_1}{N_2} = a$$


- From the above two equations,

$$\frac{v_1}{v_2} = a = \frac{i_2}{i_1} \Rightarrow v_1 i_1 = v_2 i_2$$

- Expressing these equations in effective or rms quantities,

$$\frac{V_1}{V_2} = a, \quad \frac{I_2}{I_1} = a, \quad \text{and,} \quad V_1 I_1^* = V_2 I_2^* \quad (\text{also } V_1 I_1 = V_2 I_2)$$

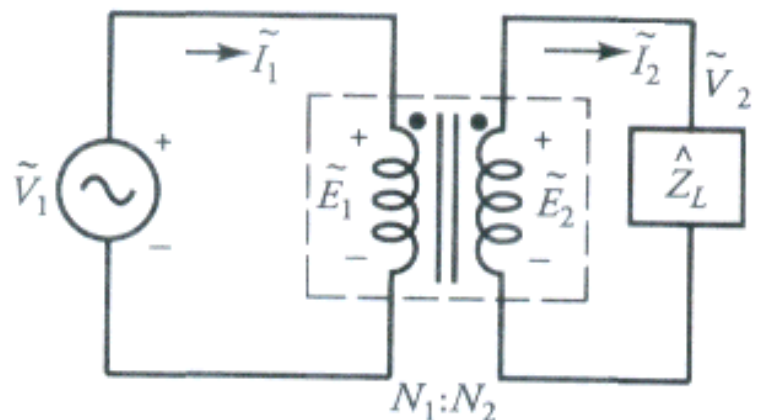
- An ideal transformer connected to a source on one side and a load on the other side can be schematically represented as shown, where



$$\frac{V_1}{V_2} = \frac{E_1}{E_2} = a, \quad \text{and} \quad \frac{I_2}{I_1} = a \Rightarrow \frac{I_2}{a} = I_1$$

REFERRED VALUES

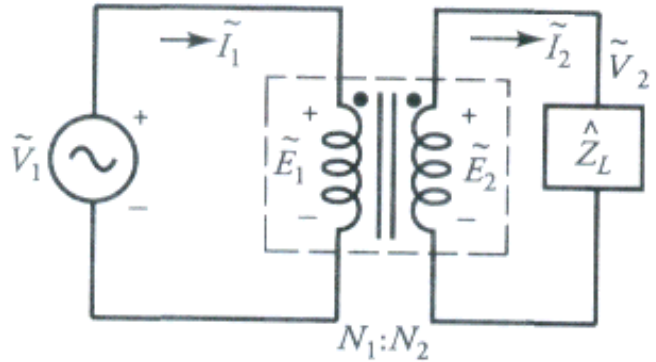- For a voltage V_2 in the secondary side of the transformer, the primary voltage will be: $V_1 = aV_2 = V_2'$ (say)



- And, for a current I_2 in the secondary side the current in the primary will be: $I_1 = I_2/a = I_2'$ (say)
- V_2' and I_2' are called the referred values of V_2 and I_2 referred to the primary side respectively.
- If Z_2 is the load impedance on the secondary side, then, $Z_2 = \frac{V_2}{I_2}$

On the primary side the impedance will appear to be:

$$Z_1 = \frac{V_1}{I_1} = \frac{aV_2}{I_2/a} = a^2 \frac{V_2}{I_2} = a^2 Z_2 = Z_2' \text{ (say)}$$

Z_2' is the referred value of Z_2 referred to the primary side.

- Similarly, V_1 , I_1 , and Z_1 when referred to the secondary side become:

$$V_1' = V_1/a, \quad I_1' = aI_1, \quad \text{and} \quad Z_1' = Z_1/a^2$$