
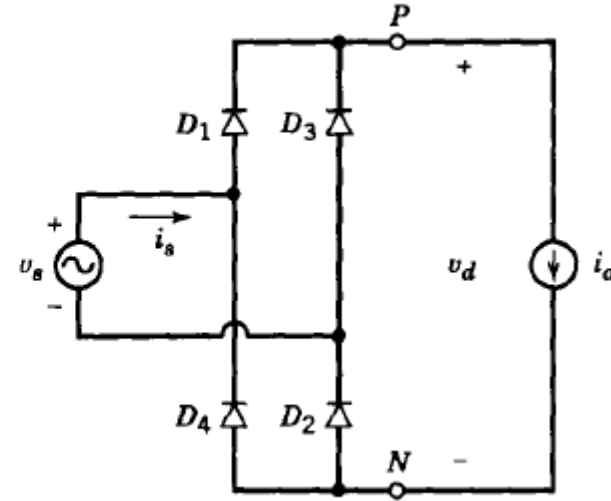


Chapter 4 Power Converters

Learning Objectives


- Understand waveforms of various circuits
- Distinguish single- and three-phase converters
- Realize effects of firing angle
- Understand operating principles of different DC/DC converters

4.1 Single-Phase Diode Bridge Rectifiers

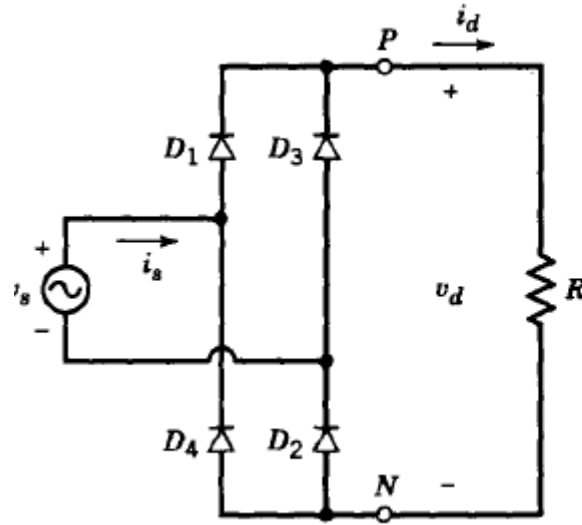

- An idealized bridge circuit with no line inductance are analysed
- A pure resistive load is very unlikely to be realized in practical case
- A constant dc current is a very good approximation in a situation when a large inductor may be connected in the circuit

4.1 Single-Phase Diode Bridge Rectifiers

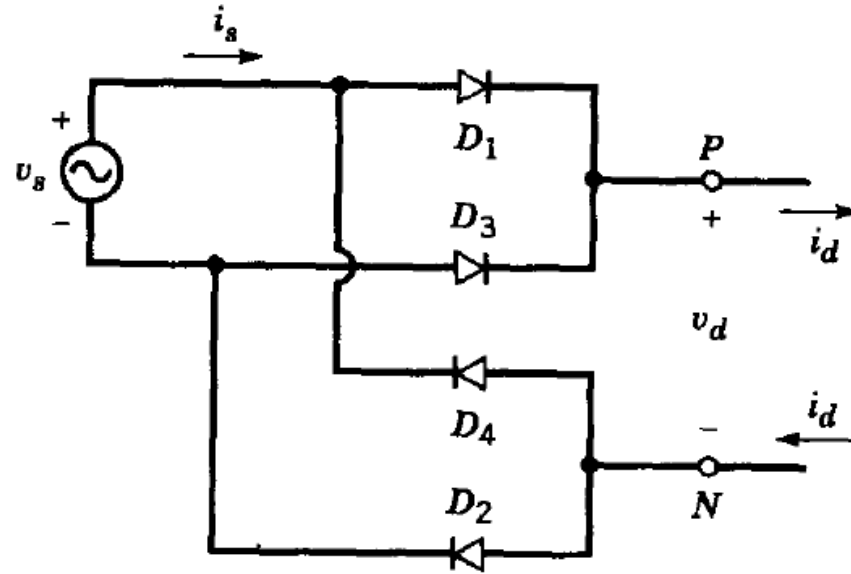



- At anytime, the dc-side output voltage is

$$v_d(t) = |v_s|$$

- Similarly, the ac-side current is

$$i_s = \begin{cases} i_d & v_s > 0 \\ -i_d & v_s < 0 \end{cases}$$

4.1 Single-Phase Diode Bridge Rectifiers

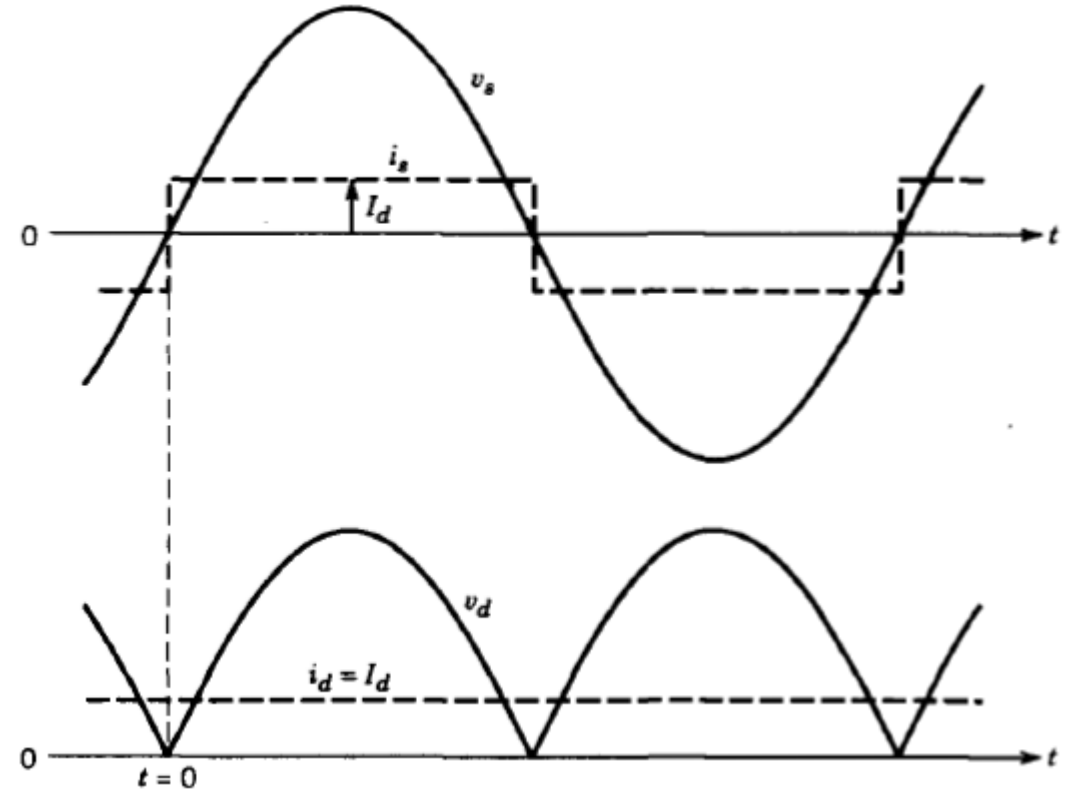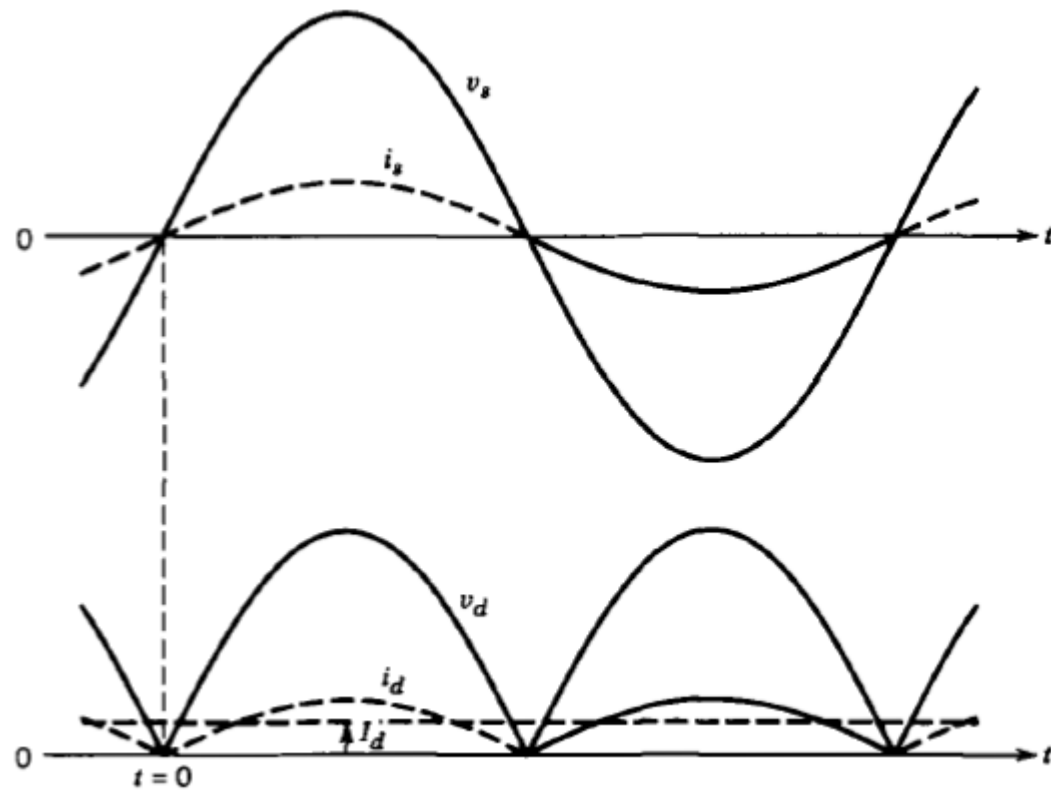

4.1 Single-Phase Diode Bridge Rectifiers

- ▶ The average output voltage is


$$V_{d0} = \frac{1}{T/2} \int_0^{T/2} \sqrt{2} V_s \sin(\omega t) dt = \frac{\sqrt{2} V_s}{\omega T/2} (\cos \omega t) \Big|_0^{T/2} = \frac{2}{\pi} \sqrt{2} V_s$$

- ▶ Hence

$$V_{d0} = \frac{2}{\pi} \sqrt{2} V_s = 0.9 V_s$$

where V_s is the rms value of the input voltage

4.2 Single-Phase Converter


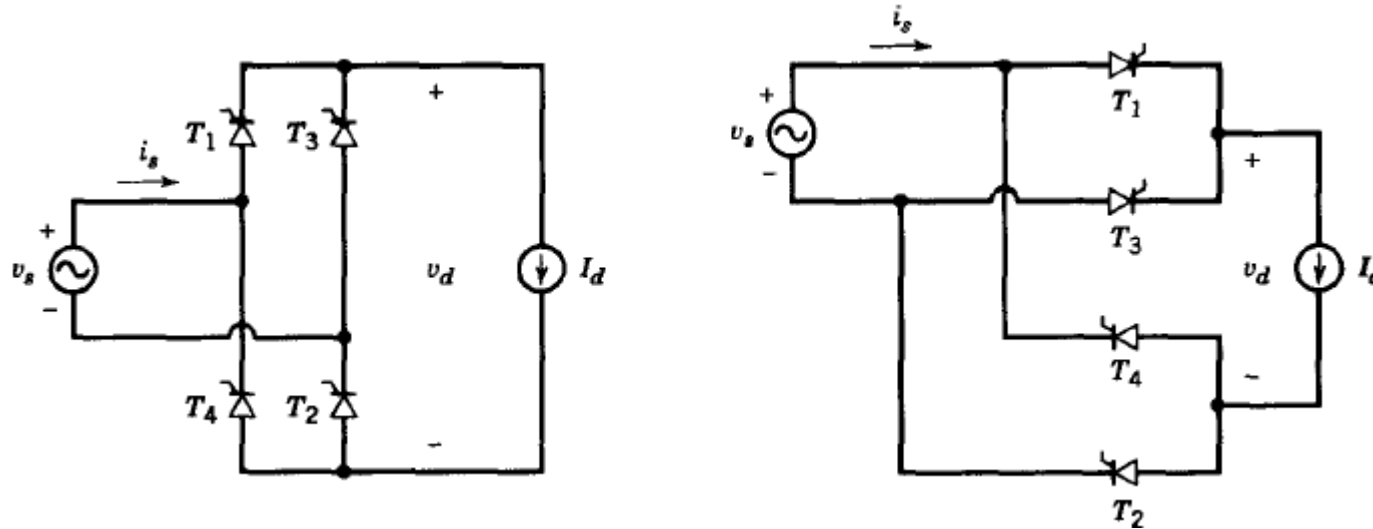


- Output voltage can be found by finding the difference between the time integral when $\alpha = 0$ and the shaded area A_α

$$V_{d\alpha} = \frac{1}{\pi} \int_{\alpha}^{\alpha+\pi} \sqrt{2}V_s \sin(\omega t) d(\omega t) = \frac{2\sqrt{2}}{\pi} V_s \cos\alpha = 0.9V_s \cos\alpha$$

- Power delivered to a constant current load can also be worked out in terms of α

4.2 Single-Phase Converter

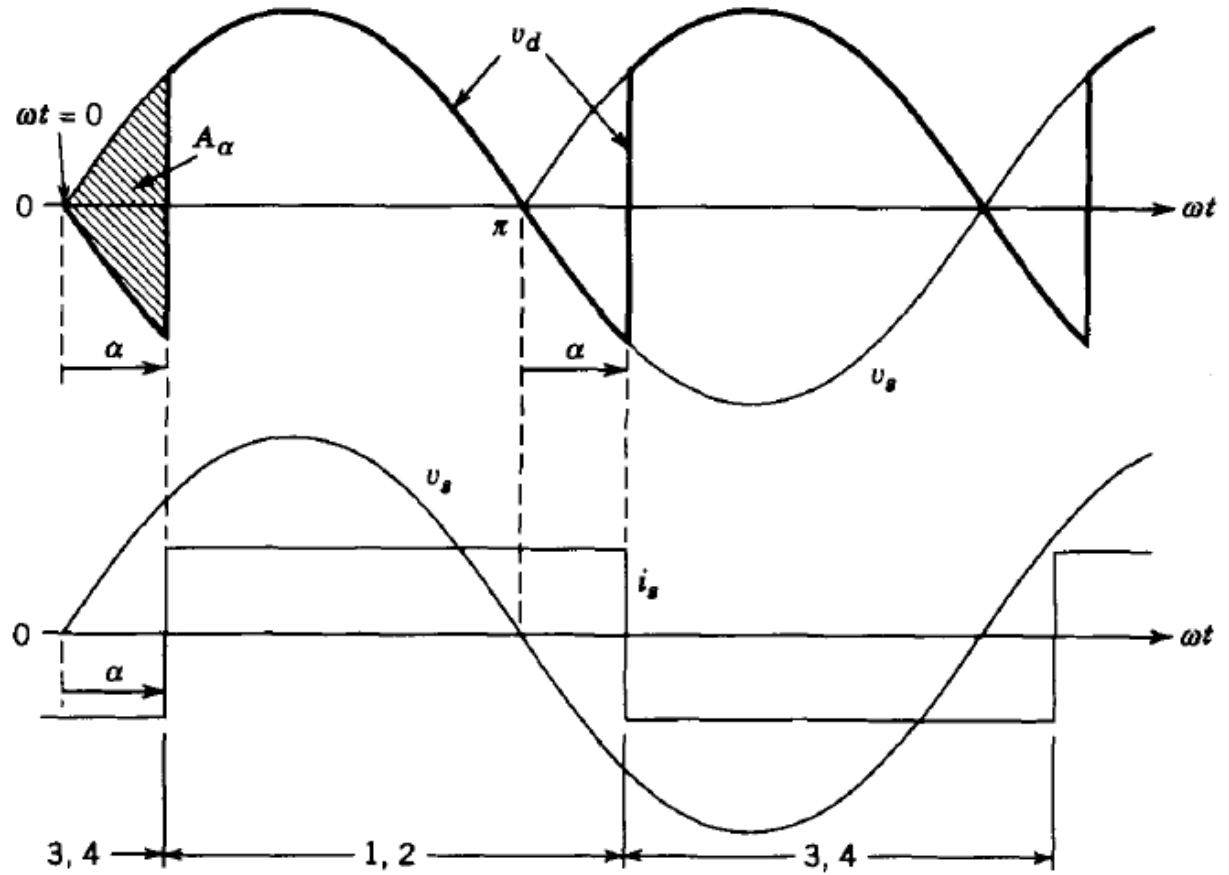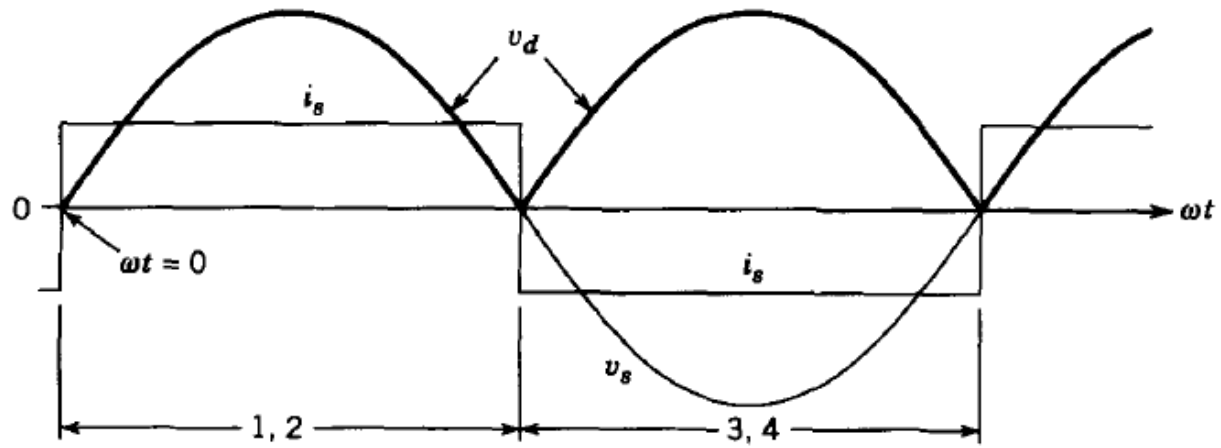

Concept Check 4.1


A separately excited DC motor, 10 hp, 220 V, 1200 rpm, is connected with an ideal single-phase full converter. Its rated armature current is 40 A with armature resistance of $0.25\ \Omega$ and armature inductance of 10 mH. The AC supply voltage is 265 V while the motor constant is 0.18 V/rpm. Assume motor current is continuous and ripple-free. If a firing angle is 30° , find

- (a) Speed of the motor (Ans: 1092.2 rpm)
- (b) Motor torque (Ans: 68.8 Nm)
- (c) Power to the motor (Ans: 8264 W)

Concept Check 4.1


Concept Check 4.1

4.3 Three-Phase, Full-Bridge Rectifier

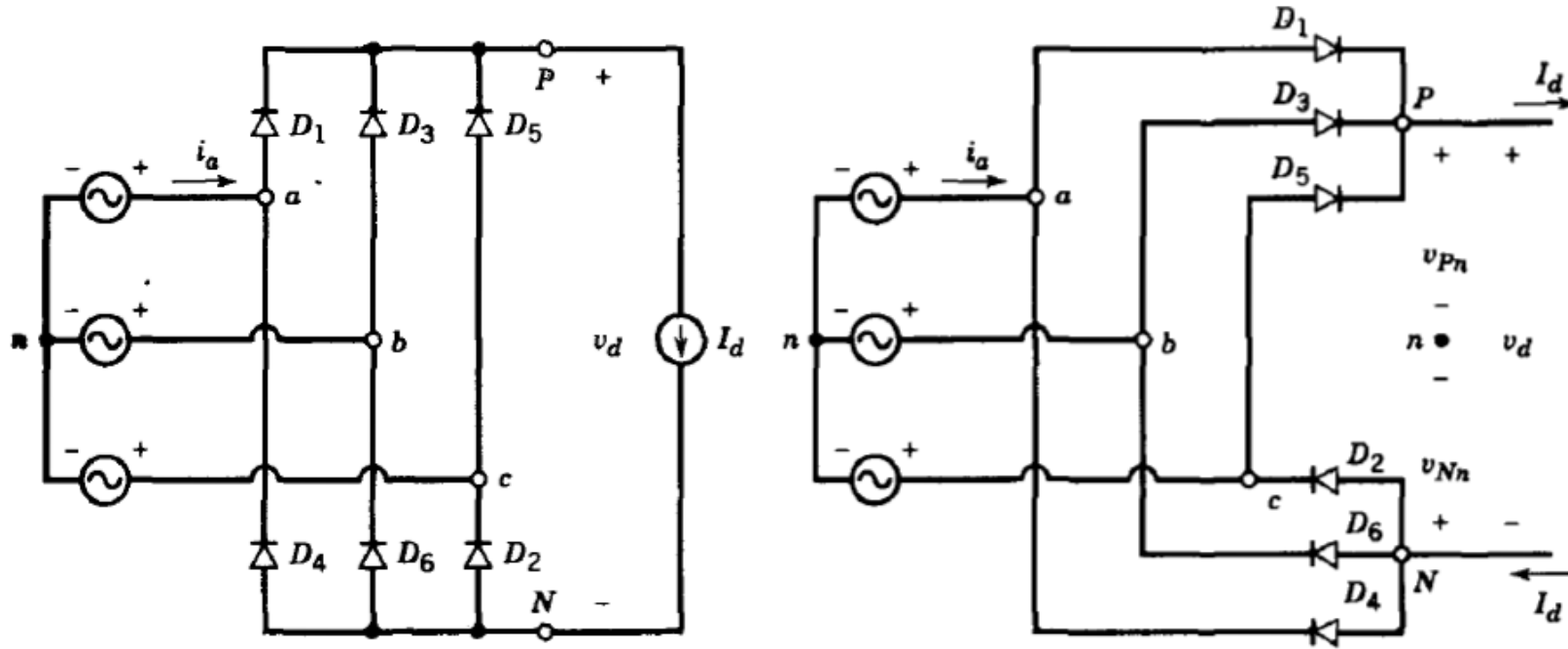

- Consider the case with no line inductance
- A 3-phase rectifier circuit somehow is similar to the case of 1-phase circuit
- A pair of diodes conduct at one time with voltage waveform across the load with respect to point n

4.3 Three-Phase, Full-Bridge Rectifier

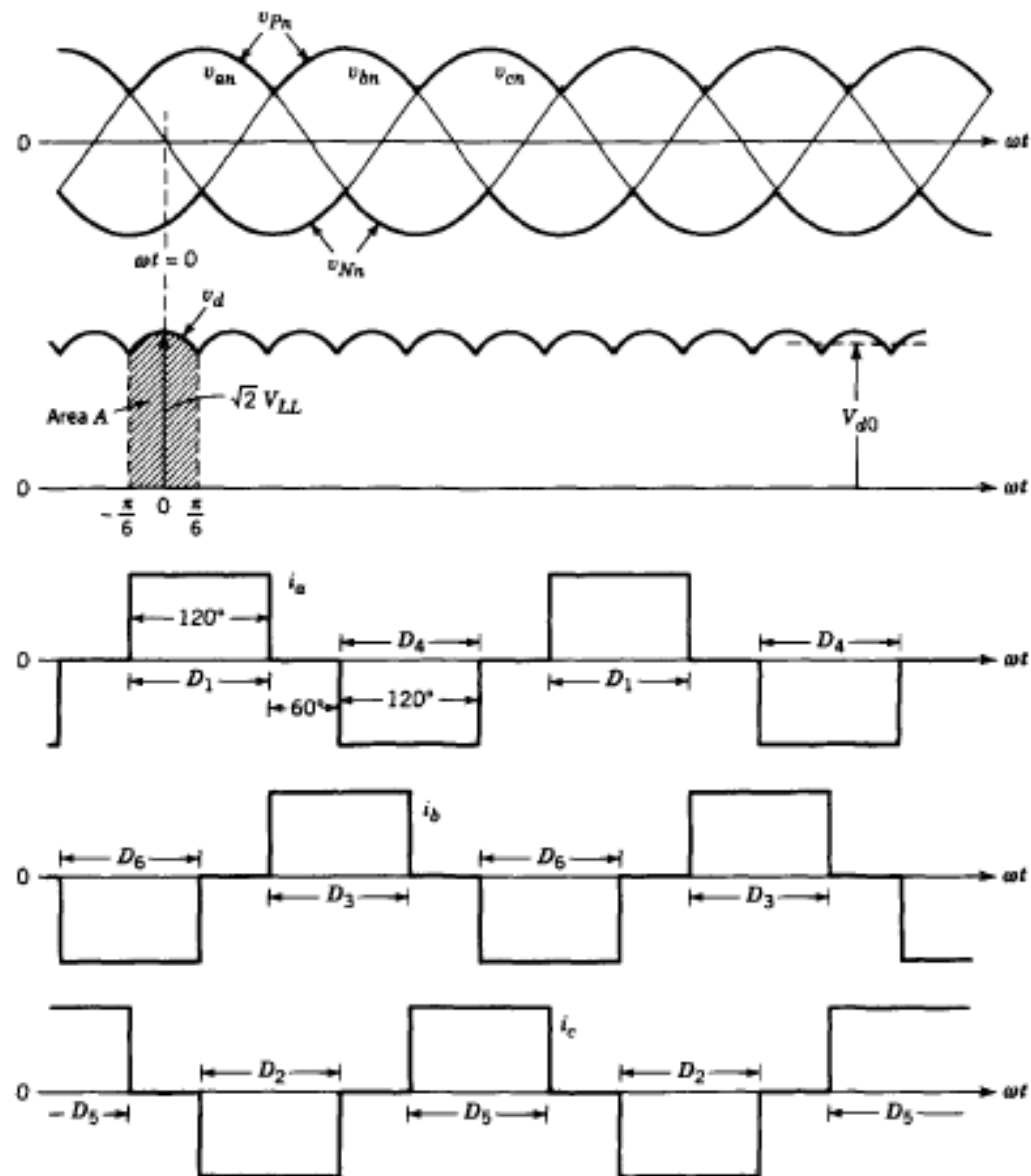

4.3 Three-Phase, Full-Bridge Rectifier

- ▶ If the same voltage waveform is modified with point N , the dc-side voltage becomes

$$v_d = v_{Pn} - v_{Nn}$$


- ▶ The instantaneous voltage waveform consists of six segment per cycle of line frequency so that it is often known as *six-pulse* rectifier
- ▶ Consider one of the six segment

$$v_d = v_{ab} = \sqrt{2}V_{LL} \cos(\omega t) \quad \text{for } -\frac{1}{6}\pi < \omega t < \frac{1}{6}\pi$$

- ▶ By integrating v_{ab} and dividing it by $\pi/3$, it yields

$$\begin{aligned} V_{d0} &= \frac{1}{\pi/3} \int_{-\pi/6}^{\pi/6} \sqrt{2}V_{LL} \cos(\omega t) d(\omega t) = \frac{3}{\pi} \sqrt{2}V_{LL} \\ &= \frac{3}{\pi} \sqrt{6}V_p \end{aligned}$$


4.4 Three-Phase Converter

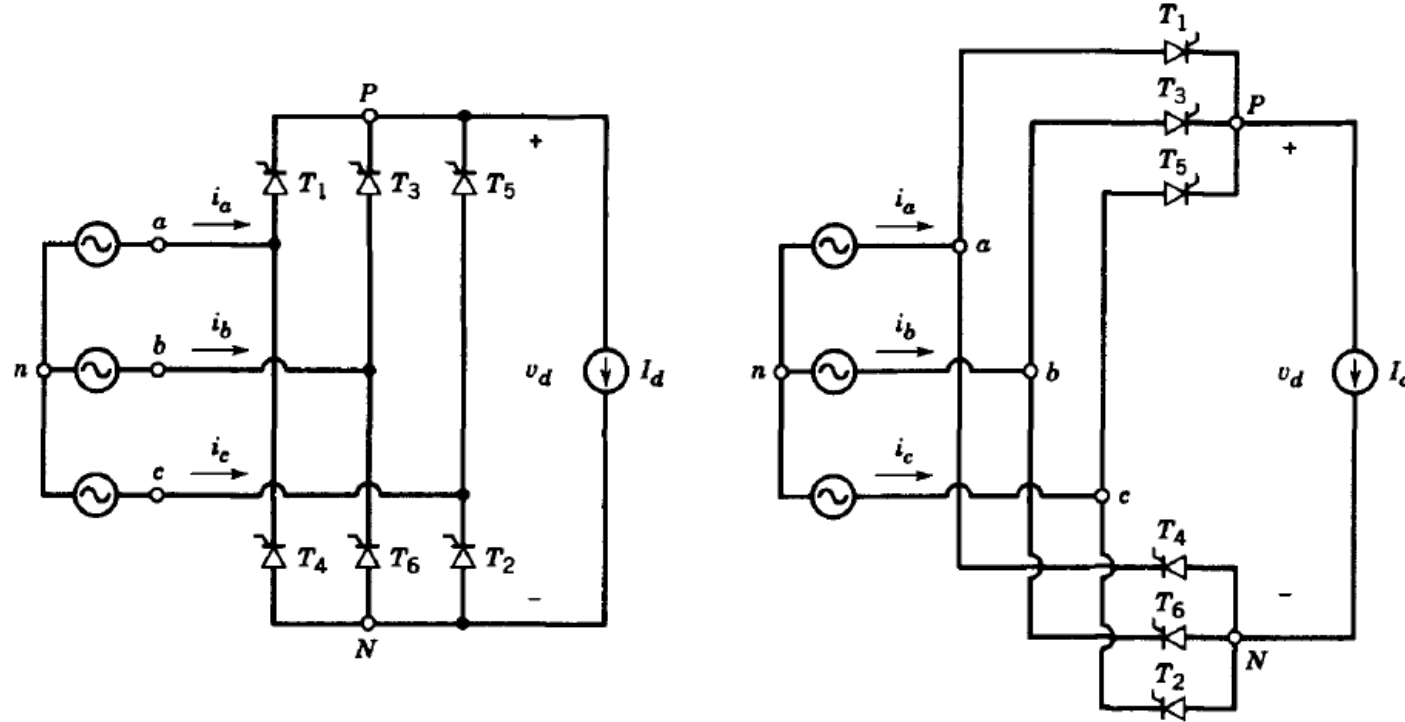

- ▶ Firing angle α results in reduction of output voltage
- ▶ Based on previous derivation

$$V_{do} = \frac{3\sqrt{2}}{\pi} V_{LL} = 1.35V_{LL}$$

4.4 Three-Phase Converter

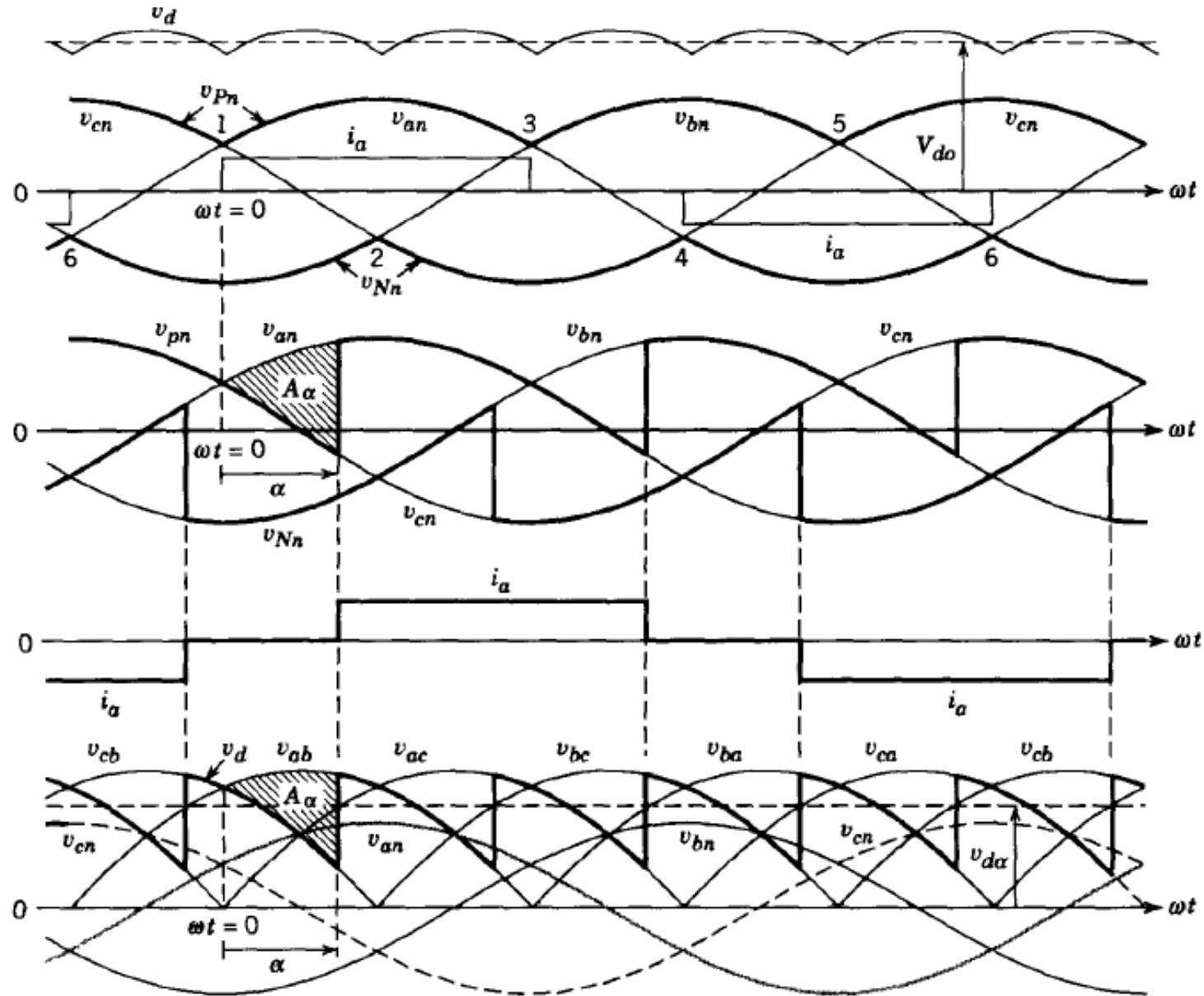

4.4 Three-Phase Converter

- ▶ Consider reduction in the average ac voltage with a delay angle

$$V_{d\alpha} = V_{do} - \frac{A_{\alpha}}{\pi/3}$$

- ▶ With reference to the waveform

$$A_{\alpha} = \int_0^{\alpha} \sqrt{2}V_{LL} \sin(\omega t) d(\omega t)$$

$$V_{d\alpha} = \frac{3\sqrt{2}}{\pi} V_{LL} \cos\alpha = 1.35V_{LL} \cos\alpha$$

Concept Check 4.2

A separately excited DC motor, 125 hp, 600 V, 1800 rpm, is connected with a three-phase full converter. The converter is operated from a three-phase, 480 V, 60 Hz supply. The rated armature current of the motor is 165 A with armature resistance of $0.0874\ \Omega$, armature inductance of 6.5 mH and motor constant is 0.33 V/rpm. Assume the converter and AC supply are ideal. If a firing angle is 30° , find



- (a) Assume at no-load condition, the armature current is 10 % of the rated current. Find no-load speeds at firing angles of 0° and 30° (Ans: 1959 rpm; 1696 rpm)
- (b) Find the firing angle for rated speed of 1800 rpm at rated motor current (Ans: 20.1°)
- (c) Find the speed regulation for the firing angle obtained in (b) (Ans: 2.18 %)

Concept Check 4.2

Concept Check 4.2

Concept Check 4.2

4.5 Step-Down (Buck) Converter

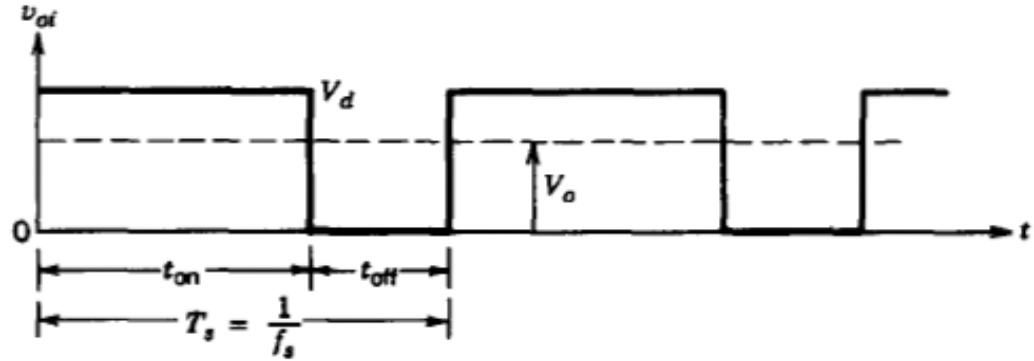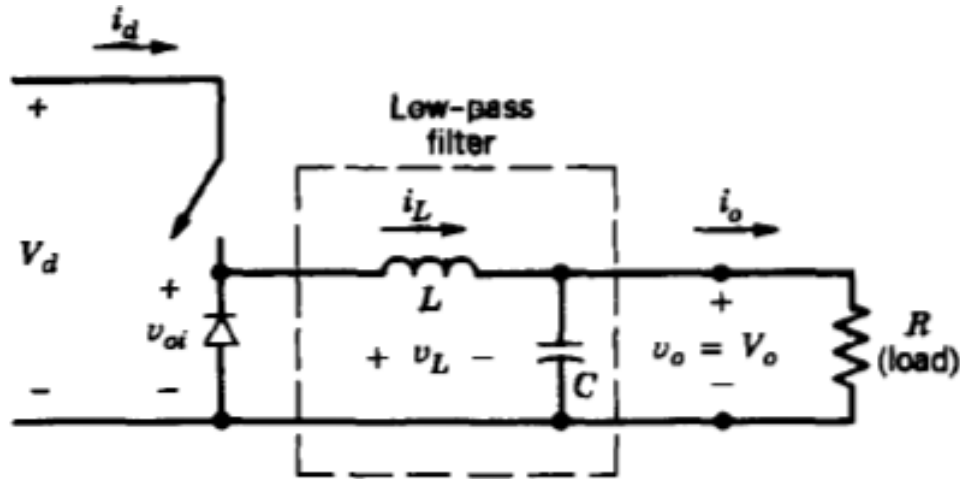


- ▶ Pulse Width Modulation (PWM) is used to control duty ratio
- ▶ Average output voltage is obtained by taking average waveform across the diode
- ▶ There are two operating modes, namely continuous conduction mode (CCM) and discontinuous conduction mode (DCM)
- ▶ In CCM, current in the inductor does not go to zero at any time

4.5 Step-Down (Buck) Converter

- Relation between output and input

$$\frac{V_o}{V_d} = D$$

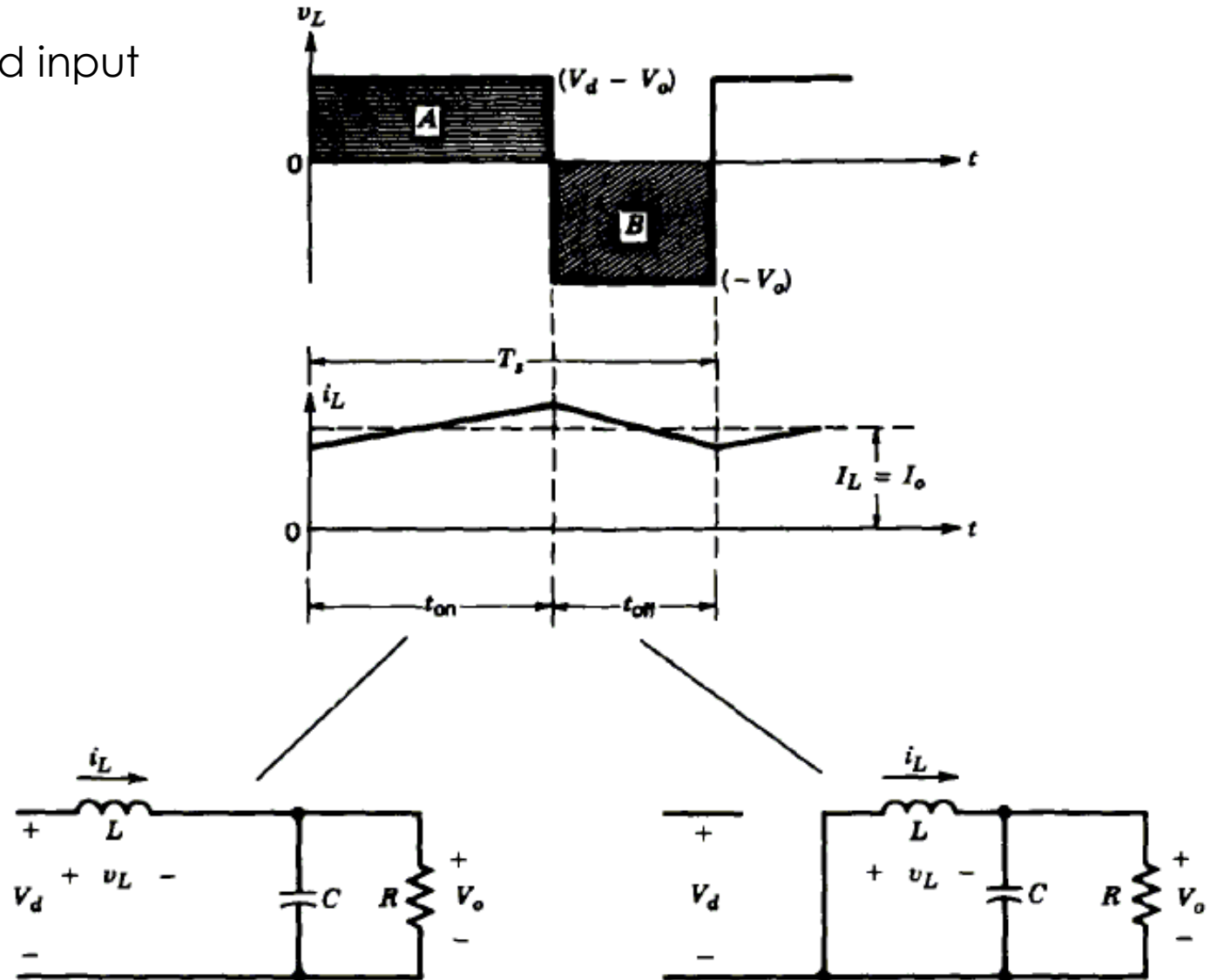

Concept Check 4.3


A separately excited DC motor is controlled by a chopper with DC supply of 120 V. The motor consists of armature resistance of $0.5\ \Omega$, armature inductance of 20 mH and motor constant is 0.05 V/rpm. The motor drives a constant-torque load that needs an average armature current of 20 A. Assume the motor current is continuous.

- (a) Find the range of speed control (Ans: $0 < N < 2200$ rpm)
- (b) Find the duty cycle (Ans: $1/12 < D < 1$)

Concept Check 4.3

Concept Check 4.3

4.6 Step-Up (Boost) Converter

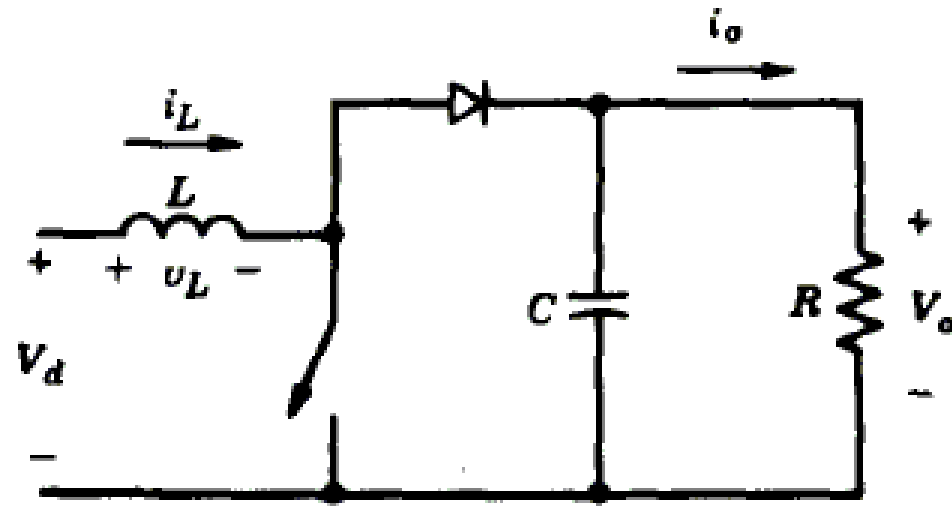


- Same as buck converter, PWM is used to control duty ratio
- Boost converter is able to produce an output voltage higher than its input
- Similar as buck converter, boost converter can also provide CCM and DCM

4.6 Step-Up (Boost) Converter

- Relation between output and input

$$\frac{V_o}{V_d} = \frac{1}{1 - D}$$

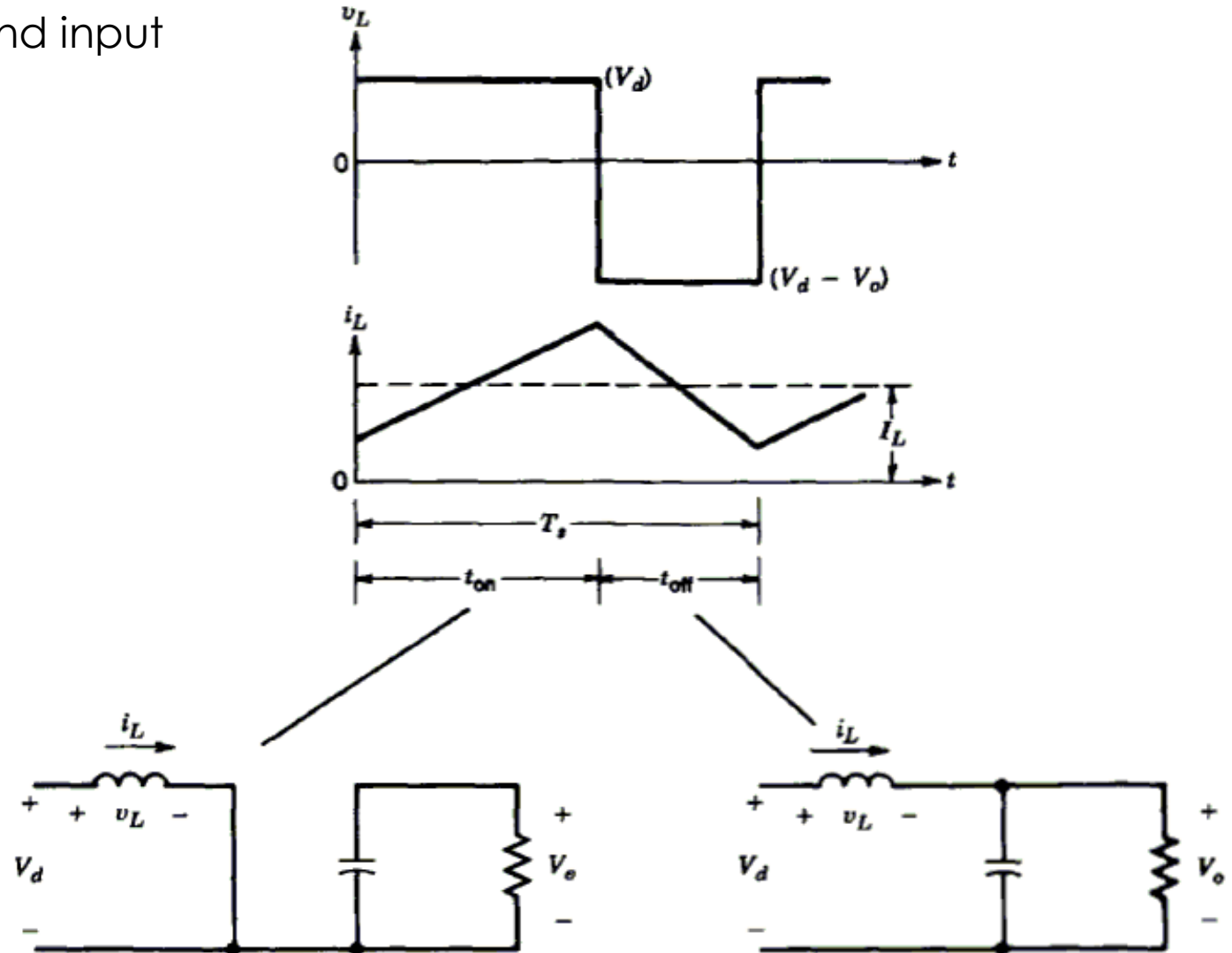


Concept Check 4.4

A step-up converter is used to control a motor during regenerative braking mode. The motor consists of voltage constant of 0.3 V/rpm and DC bus voltage of 600 V . When the motor is at 800 rpm , it draws average motor current of 300 A .

- (a) Draw the waveforms of output voltage, output current and supply current.
- (b) Find the duty ratio of the converter.
- (c) Find the power fed back to the supply.


Concept Check 4.4

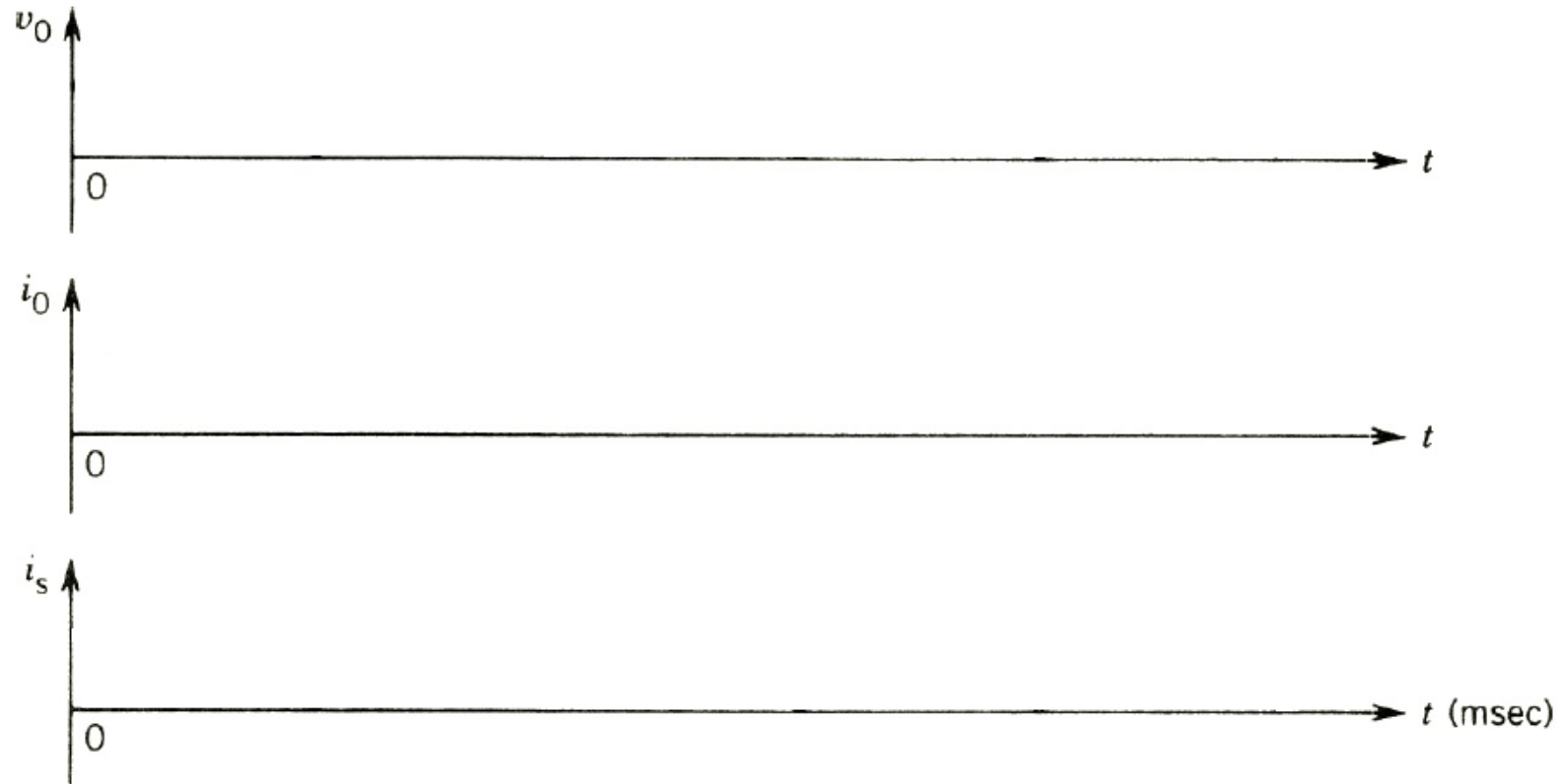

Concept Check 4.4

Concept Check 4.4

4.7 Buck-Boost Converter


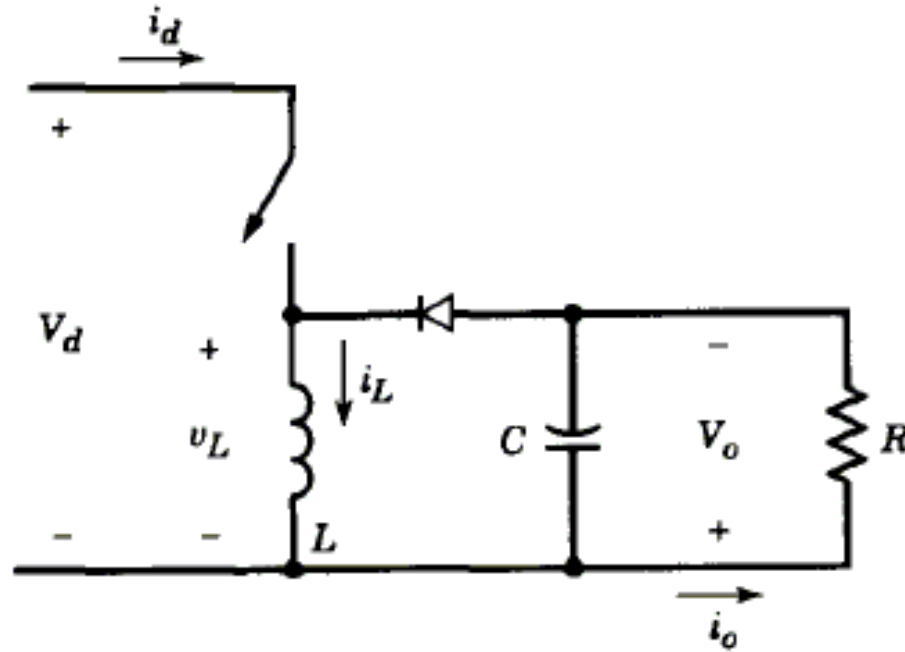


- ▶ A buck-boost converter is able to produce an output voltage higher or lower than its input with the polarity reversed
- ▶ When switch is closed, input provides energy to inductor and diode is reversed biased
- ▶ When the switch is open, the stored energy is transferred to the output
- ▶ No energy is supplied by the input during this interval


4.7 Buck-Boost Converter

- Relation between output and input

$$\frac{V_o}{V_d} = \frac{D}{1 - D}$$

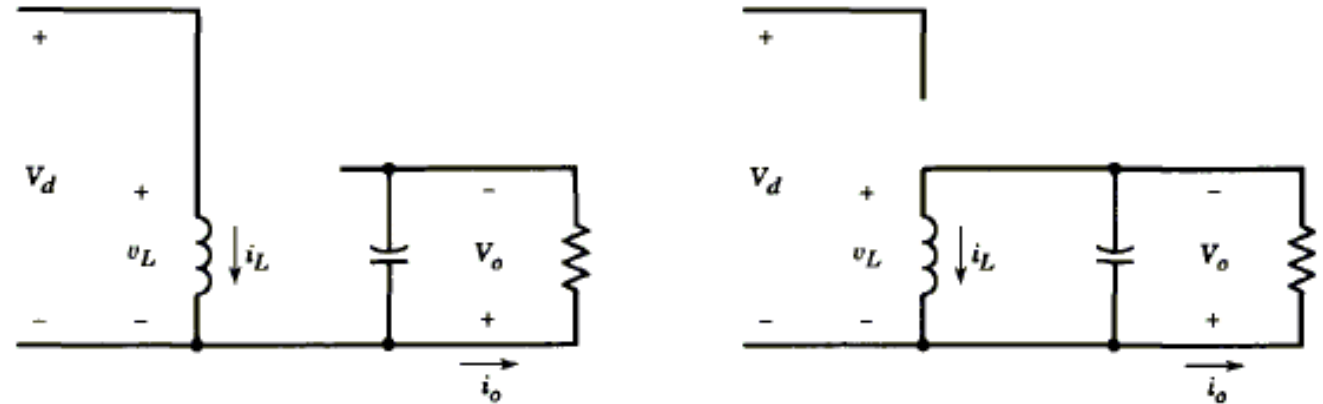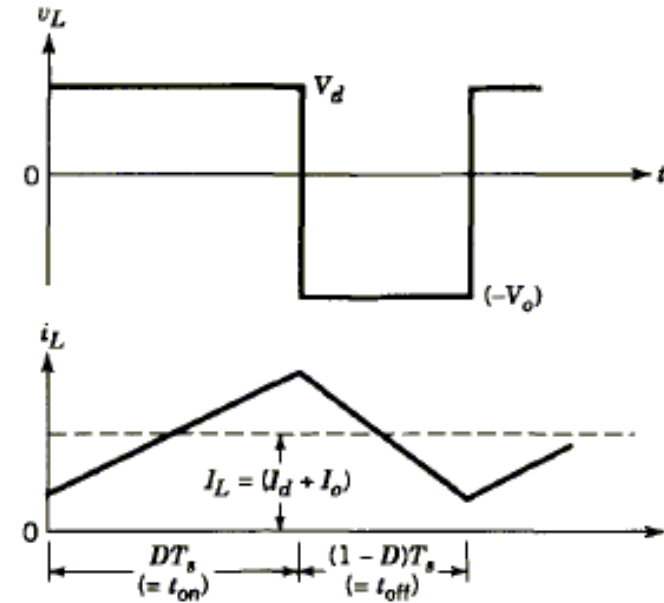


4.8 Two-Quadrant Chopper

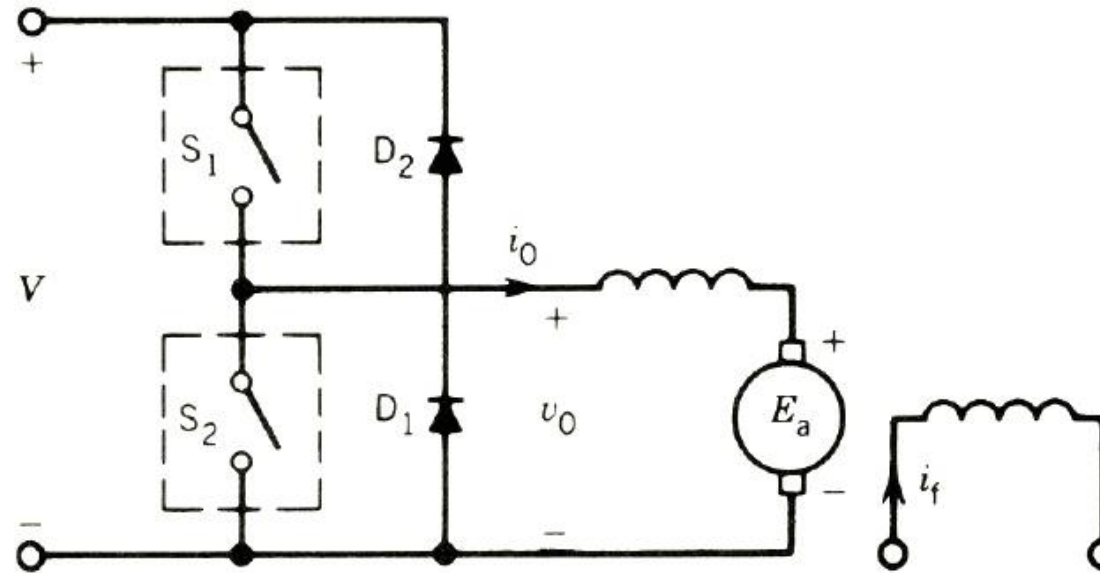

- Two-quadrant chopper is formed by combination of buck and boost converters
- If S_1 and D_1 are operated, the system will operate as a buck converter and the DC machine as a motor
- If S_2 and D_2 are operated, the system will operate as a boost converter and the DC machine as a generator

4.8 Two-Quadrant Chopper

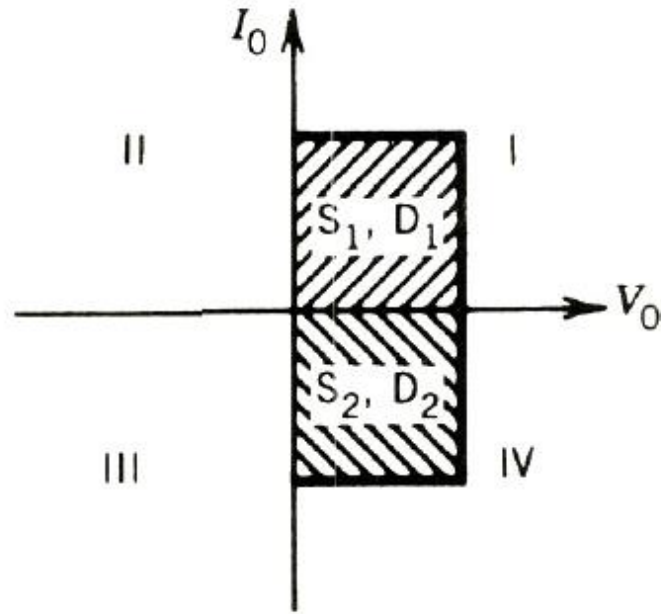

- When the chopper is as a buck converter, its output voltage is either V or zero
- Its average voltage output is positive with output current flows in positive direction
- When the chopper is as a boost converter, its output voltage is either zero or V
- Its average voltage output is positive with output current flows in negative direction