

### **Problem Set 3 DC Machines**

1. Consider a 240 V separate excited DC motor with an armature resistance of  $0.06\ \Omega$ . When it is connected to a 240 V supply, it can draw 90 A and rotates at 1200 rpm.
  - a. Find the developed torque at this operating condition.
  - b. Under same excitation, if the developed torque is 280 Nm, find the speed and armature current.
2. Consider a 25 kW, 120 V separately excited DC machine with an armature resistance of  $0.025\ \Omega$ . When it is operated with a constant field current and constant speed of 2500 rpm, its open circuit armature voltage becomes 120 V.
  - a. If the DC machine is connected to a 125 V supply, will it operate as a generator or a motor?
  - b. Find the armature current, supply power and developed torque.
  - c. Repeat (a) and (b) if the DC machine is connected to a 115 V supply.
3. A DC machine is connected across a 240-volt line. It rotates at 1200 rpm and produces 230 V with armature current of 40 A.
  - a. Is the machine operating as a generator or a motor?
  - b. Find the resistance of the armature circuit, power losses in armature circuit resistance, electromagnetic power and electromagnetic torque.
4. A 500 V DC shunt motor consists of an armature resistance of  $0.25\ \Omega$  and field resistant of  $240\ \Omega$ . It drives a mechanical load that needs a torque proportional to speed. When the system is connected to a 500 V supply, it takes 100 A and rotates at 1100 rpm. By inserting a resistance in series with the armature, the speed is able to reduce to 900 rpm. Find the value of the added series resistance.
5. A 125 V, 5 kW, 1800 rpm DC shunt motor needs only 5 V to send full-load current through the armature when the armature is held stationary.
  - a. If full-line voltage is impressed across the armature at starting, find the armature current.
  - b. If the starting current is limited to 1.5 times of the full-load current, find the value of the external resistance needed.
  - c. Neglect rotational losses and assume 10 % reduction due to armature reaction at full load.
    - i. The motor is coupled to a mechanical load by a belt. Find the generated voltage at full-load conditions.
    - ii. If the belt breaks, find the speed of the motor.

Answer

1. (a) 168.3 Nm                      (b) 123.5 rad/s; 149.7 A
2. (a) Motor                      (b) 200 A; 25 W; 91.7 Nm                      (c) Generator; 200 A; 23 kW; 91.7 Nm
3. (b) 0.25  $\Omega$ ; 400 W; 9200 W; 73.2 Nm                      (ci) 1252 rpm                      (cii) 1127 rpm
4. 1.11  $\Omega$
5. (a) 40 A                      (b) 1.96  $\Omega$                       (ci) 120 V                      (cii) 1688 rpm