

### **Problem Set 3 DC Machines**

1. Consider a 240 V separate excited DC motor with an armature resistance of  $0.06\ \Omega$ . When it is connected to a 240 V supply, it can draw 90 A and rotates at 1200 rpm.
  - a. Find the developed torque at this operating condition.
  - b. Under same excitation, if the developed torque is 280 Nm, find the speed and armature current.
2. Consider a 25 kW, 120 V separately excited DC machine with an armature resistance of  $0.025\ \Omega$ . When it is operated with a constant field current and constant speed of 2500 rpm, its open circuit armature voltage becomes 120 V.
  - a. If the DC machine is connected to a 125 V supply, will it operate as a generator or a motor?
  - b. Find the armature current, supply power and developed torque.
  - c. Repeat (a) and (b) if the DC machine is connected to a 115 V supply.
3. A DC machine is connected across a 240-volt line. It rotates at 1200 rpm and produces 230 V with armature current of 40 A.
  - a. Is the machine operating as a generator or a motor?
  - b. Find the resistance of the armature circuit, power losses in armature circuit resistance, electromagnetic power and electromagnetic torque.
4. A 500 V DC shunt motor consists of an armature resistance of  $0.25\ \Omega$  and field resistant of  $240\ \Omega$ . It drives a mechanical load that needs a torque proportional to speed. When the system is connected to a 500 V supply, it takes 100 A and rotates at 1100 rpm. By inserting a resistance in series with the armature, the speed is able to reduce to 900 rpm. Find the value of the added series resistance.
5. A 125 V, 5 kW, 1800 rpm DC shunt motor needs only 5 V to send full-load current through the armature when the armature is held stationary.
  - a. If full-line voltage is impressed across the armature at starting, find the armature current.
  - b. If the starting current is limited to 1.5 times of the full-load current, find the value of the external resistance needed.
  - c. Neglect rotational losses and assume 10 % reduction due to armature reaction at full load.
    - i. The motor is coupled to a mechanical load by a belt. Find the generated voltage at full-load conditions.
    - ii. If the belt breaks, find the speed of the motor.

### Answer

1.

$$(a) E_a = 240 - 90 \times 0.06 = 240 - 5.4 = 234.6V$$

$$\text{speed } \omega = \frac{1200}{60} \times 2\pi = 40\pi \text{ rad/sec}$$

$$k_a \phi = \frac{E_g}{\omega} = \frac{243.6}{40\pi} = 1.87V \cdot s/\text{rad}$$

$$T = k_a \phi I_a = 1.87 \times 90 = 168.3N \cdot m$$

$$(b) I_a = \frac{T}{k_a} = \frac{280}{1.87} = 149.7A$$

$$E_g = 240 - 149.7 \times 0.06 = 240 - 8.98 = 231V$$

$$\omega = \frac{231}{1.87} = 123.53 \text{ rad/sec}$$

$$n = \frac{60 \times \omega}{2\pi} = 1180.2 \text{ rpm}$$

2.

$$(a) V_a = 125V, E_g = 120V$$

$V_a > E_g \rightarrow$  machine is operating as a motor

$$I_a = \frac{125 - 120}{0.025} = 200A$$

$$P_{in} = 125 \times 200 = 25kW$$

$$P_g = 120 \times 200 = 24kW$$

$$\omega_m = \frac{2500}{60} \times 2\pi = 261.7 \text{ rad/sec}$$

$$T = \frac{P_g}{\omega_m} = \frac{24000}{261.7} = 91.7N \cdot m$$

$$(b) V_a = 125V, E_g = 120V$$

$V_a < E_g \rightarrow$  machine is operating as a generator

$$I_a = \frac{120 - 115}{0.025} = 200 \text{ A}$$

$$P_{\text{in}} = 115 \times 200 = 23 \text{ kW}$$

$$P_g = 120 \times 200 = 24 \text{ kW}$$

$$\omega_m = \frac{2500}{60} \times 2\pi = 261.7 \text{ rad/sec}$$

$$T = \frac{P_g}{\omega_m} = \frac{24000}{261.7} = 91.7 \text{ N} \cdot \text{m}$$

3.

$$(a) \quad V_t < E_a \rightarrow I_a \text{ into the machine}$$

$\rightarrow$  motor

$$(b) \quad R_a = \frac{240 - 230}{40} = 0.25 \text{ A}$$

$$(c) \quad I_a^2 R_a = 40^2 \cdot 0.25 = 400 \text{ W}$$

$$E_a I_a = 230 \cdot 40 = 9200 \text{ W}$$

$$(d) \quad \omega_m = \frac{1200}{60} \cdot 2\pi = 125.7 \text{ rad/sec}$$

$$(e) \quad T = \frac{9200}{125.7} = 73.19 \text{ N} \cdot \text{m}$$

4.

$$E_a|_{1100} = 500 - 100 \cdot 0.25 = 475 \text{ V}$$

$$E_a|_{900} = 475 \cdot \frac{900}{1100} = 388.6 \text{ V}$$

$$I_a|_{1100} = 100 \text{ A}$$

$$I_a|_{900} = 100 \cdot \frac{900}{1100} = 81.8 \text{ A}$$

$$IR = V - E_a = 500 - 388.6 = 111.4 \text{ V}$$

$$R = \frac{111.4}{81.8} = 1.36 \Omega$$

$$R_{\text{series}} = 1.36 - 0.25 = 1.11 \Omega$$

5.

$$(a) \quad R_a = \frac{5}{40} = 0.125\Omega, I_a = \frac{125}{0.125} = 1000A$$

$$I_{a(\text{rated})} = \frac{5000}{125} = 40A$$

$$(b) \quad I_a = 40 \times 1.5 = \frac{125}{0.125 + R_{\text{ex}}} \rightarrow R_{\text{ex}} = 1.9583\Omega$$

$$(c) \quad E_a = 125 - 40 \times 0.125 = 120V$$

$$125 = k_a \phi n$$

$$120 = k_a (0.9\phi) 1800$$

$$n = \frac{125}{120} \times 0.9 \times 1800 = 1687.5\text{rpm}$$