
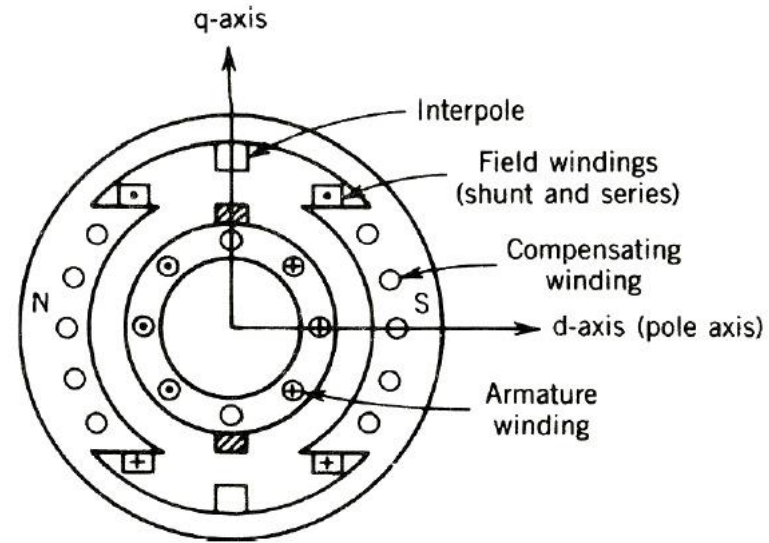


# Chapter 3 DC Machines

## Learning Objectives


- Know fundamental equations for DC machines
- Classify different types of DC machines
- Understand types of speed controls

## 3.1 Fundamentals

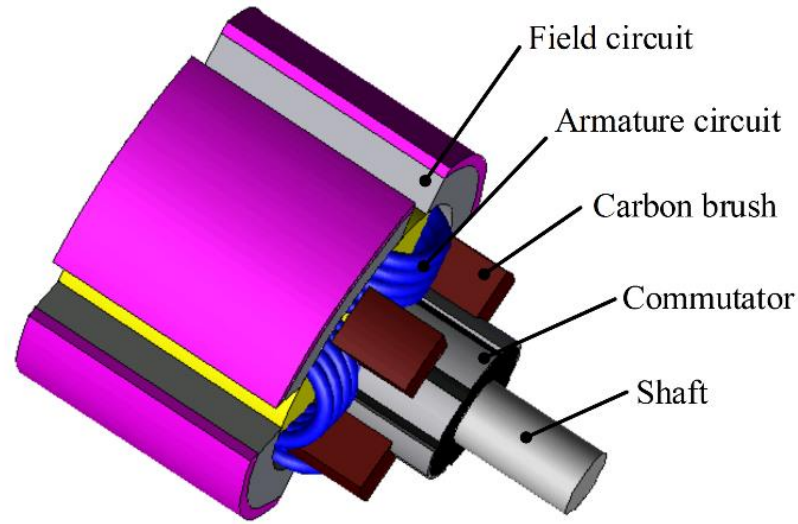


- It consists of stator, rotor, commutator and carbon brushes
- The stator is field circuit that incorporates field windings or permanent-magnets (PMs) in order to produce magnetic flux
- The rotor is armature circuit that installs with armature winding
- Upon support by commutator and carbon brushes, the armature current can be switched to flow in bidirectional form

## 3.1 Fundamentals

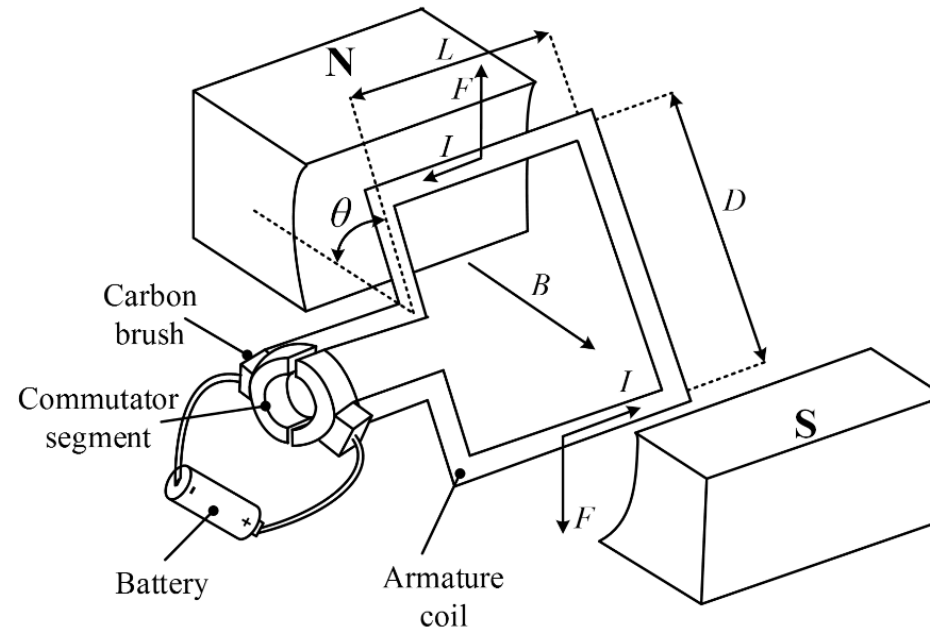


- ▶ A basic two-pole DC machine is used for illustration
- ▶ The armature circuit consists of a simple single-turn coil that is connected to the DC source via a two-segment commutator and a pair of carbon brushes
- ▶ The commutator serves to reverse the direction of current flow
- ▶ The carbon brushes enables electrical conduction between the rotating commutator and the stationary DC source

## 3.2 Operating Principle

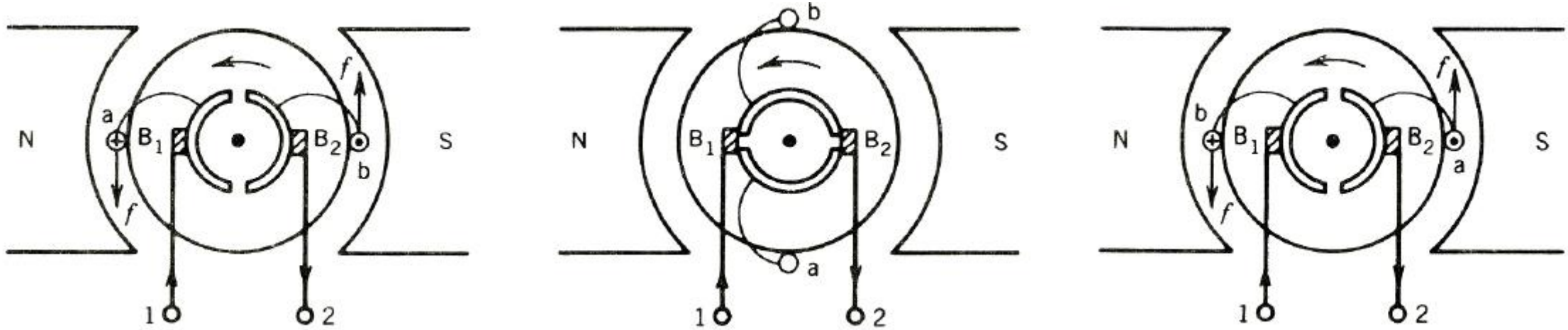


- Field windings is placed on the stator while armature winding is on rotor
- Current will be fed into the armature through the brushes
- Current will reverse when the turn passes the interpolar where the commutator segments touches the other brushes

## 3.2 Operating Principle

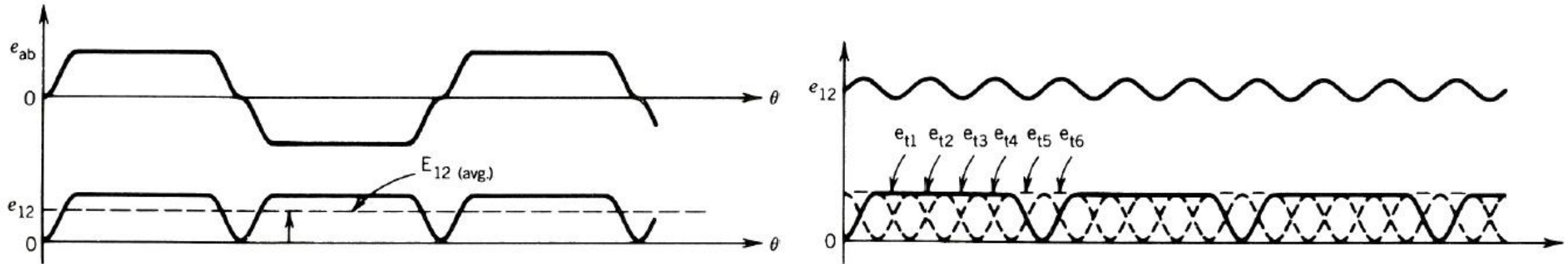

- Even though the voltage induced in the turn is alternating, the voltage at the brush terminal is unidirectional
- This unidirectional voltage generally consists of large ripple
- In order to reduced ripples, a large number of turns are placed in several slots


## 3.2 Operating Principle

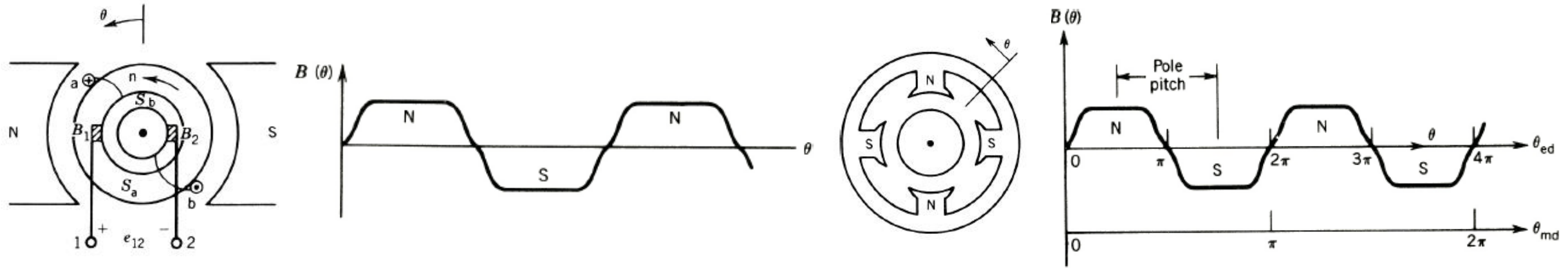

- ▶ The resultant MMF wave can make one revolution per cycle of current variation in a two-pole machine
- ▶ In a  $p$ -pole machine, one cycle of current variation will make MMF wave instead rotate by  $2 / p$  revolutions
- ▶ Distance between the centers of two adjacent poles is known as *pole pitch*

$$\text{One pole pitch} = 180^\circ_{ed} = \frac{360^\circ_{md}}{p}$$

## 3.2 Operating Principle

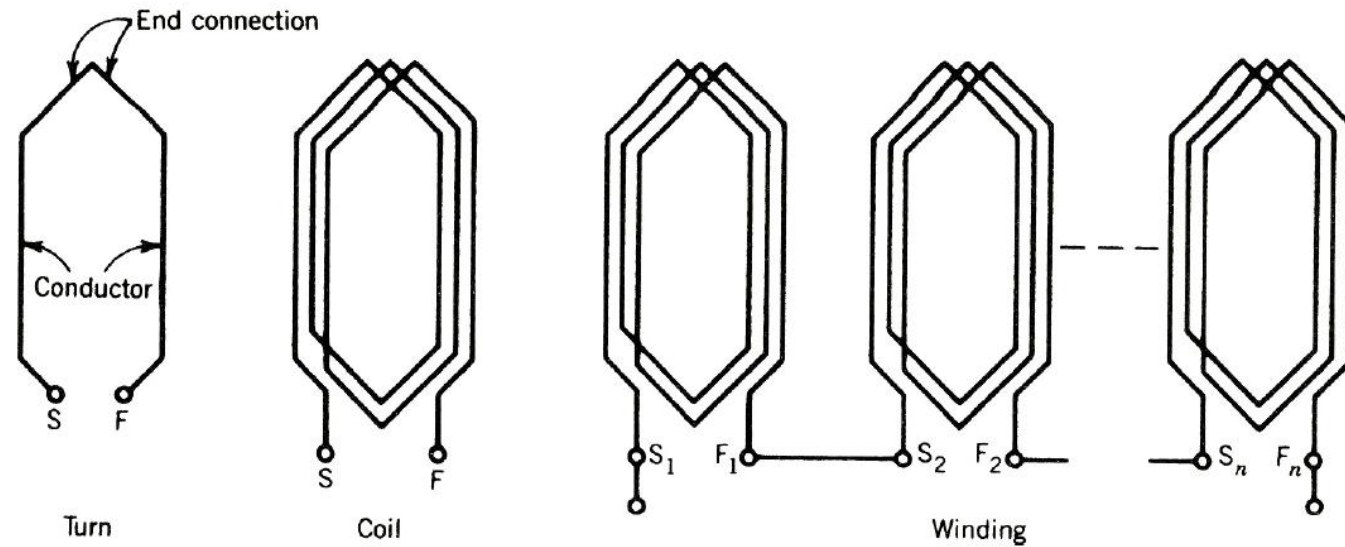

- ▶ A turn means two conductors are connected to one end by an other
- ▶ A coil means several turns are connected in series
- ▶ A winding means several coils are connected in series

## 3.2 Operating Principle

- ▶ According to Faraday's Law, average value of induced voltage

$$\begin{aligned}\bar{e}_t &= \overline{2B(\theta)l\omega_m r} \\ &= \frac{\Phi p}{\pi} \omega_m\end{aligned}$$

- ▶ Assume total of turns  $N$  in the armature winding, voltage induced in all the turns connected in series for one parallel path  $a$  will contribute average terminal voltage

$$\begin{aligned}E_a &= \frac{N}{a} \bar{e}_t \\ &= \frac{Np}{\pi a} \Phi \omega_m \\ &= K_a \Phi \omega_m\end{aligned}$$



## 3.2 Operating Principle

- ▶ Force acting on a conductor

$$f_c = B(\theta)l \frac{I_a}{a}$$

- ▶ Average torque produced by a conductor

$$\bar{T}_c = \frac{\Phi I_a}{2\pi a}$$

- ▶ Total torque by all conductors in the armature windings

$$\begin{aligned} T &= 2NT_c = \frac{N\Phi I_a}{\pi a} \\ &= K_a \Phi I_a \end{aligned}$$

- ▶ Energy conversion can be described as

$$E_a I_a = K_a \Phi \omega_m I_a = T \omega_m$$

## Concept Check 3.1

A four-pole DC machine consists of an armature of radius of 12.5 cm and effective length of 25 cm. The poles cover 75 % of the armature periphery. The armature windings consist of 33 coil, with each coil of 7 turns. The coils are accommodated in 33 slots. The average flux density in each pole is 0.75 T.







- (a) Find the armature constant  $K_a$  (Ans: 73.53)
- (b) Find the induced armature voltage when it rotates at 1000 rpm (Ans: 212.5 V)
- (c) Find the electromagnetic torque when the armature current is 400 A (Ans: 811.8 Nm)
- (d) Find the power developed by the armature (Ans: 85 kW)

# Concept Check 3.1


# Concept Check 3.1
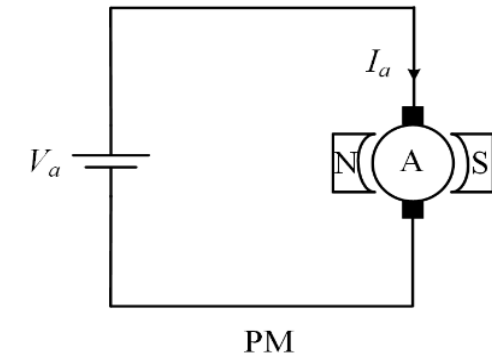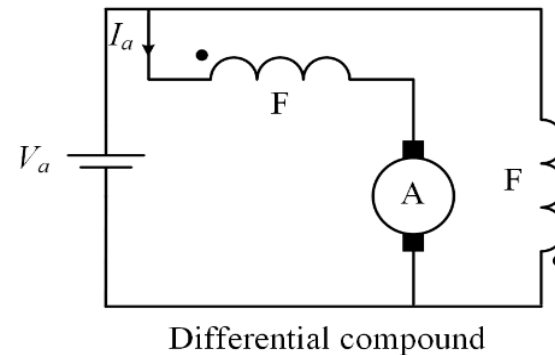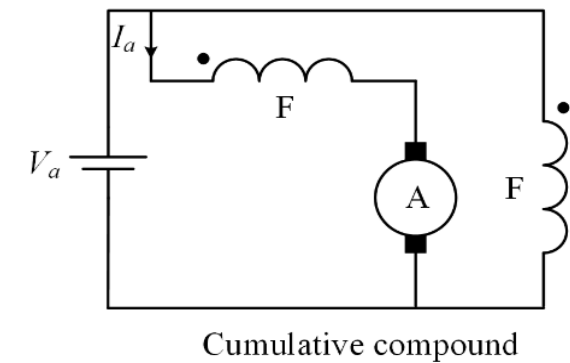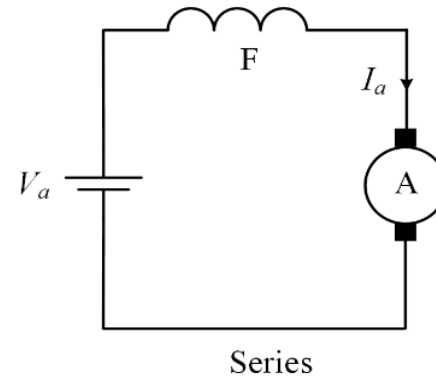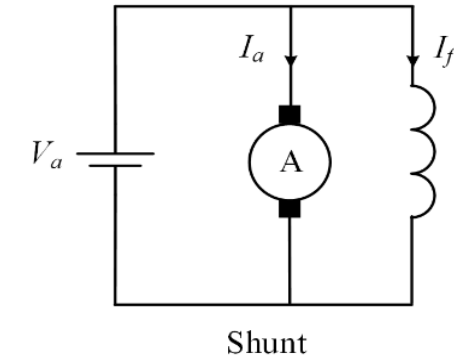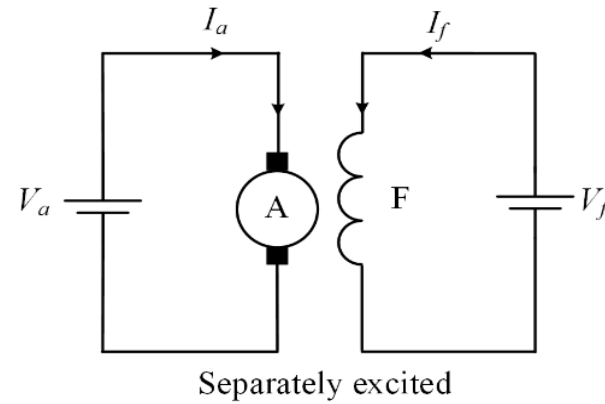
### 3.3 Types of DC Machines

- Separately excited DC
- Series DC
- Shunt DC
- Cumulative compound DC
- Differential compound DC
- Permanent-magnet DC



### 3.4 Separately Excited DC Machine

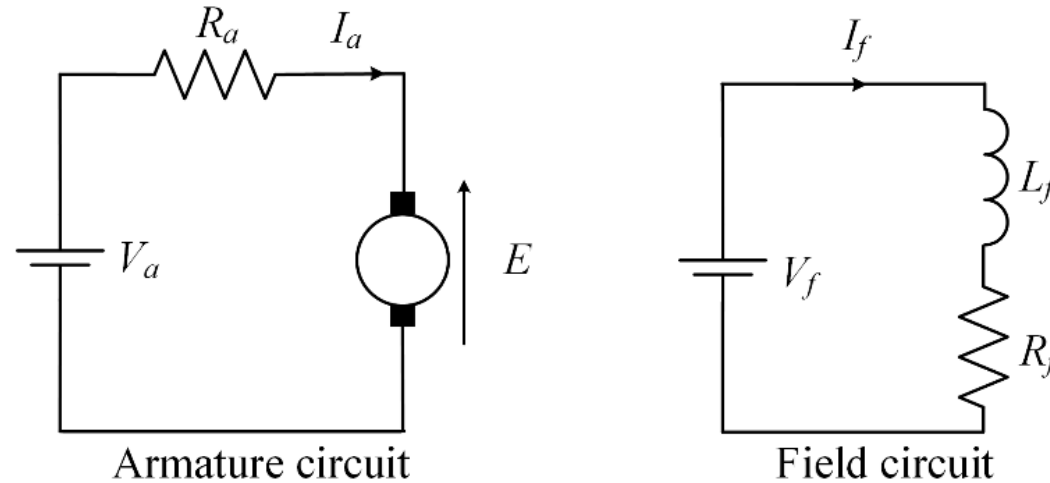

- A separately excited DC machine is used for illustration
- Consider magnetic flux generated by field circuit is

$$\Phi = K_f I_f$$

where  $K_f$  is field constant

## 3.4 Separately Excited DC Machine

- ▶ Back electromotive force (EMF) generated in DC machine becomes

$$E_a = K_a \Phi \omega_m = K_v I_f \omega_m$$

where  $K_a$  is armature constant

$K_v$  is voltage constant

- ▶ Hence, armature voltage becomes

$$V_a = \pm E_a + R_a I_a$$

where + is for motor while – is for generator

- ▶ Meanwhile, generated torque from excitation of field circuit is

$$T_e = K_a \Phi I_a = K_t I_f I_a$$

where  $K_t$  is torque constant

- ▶ Output power can be


$$P = T_e \omega_m$$

Motoring

$$P = V_a I_a$$

Regenerative

### 3.5 Armature Reaction

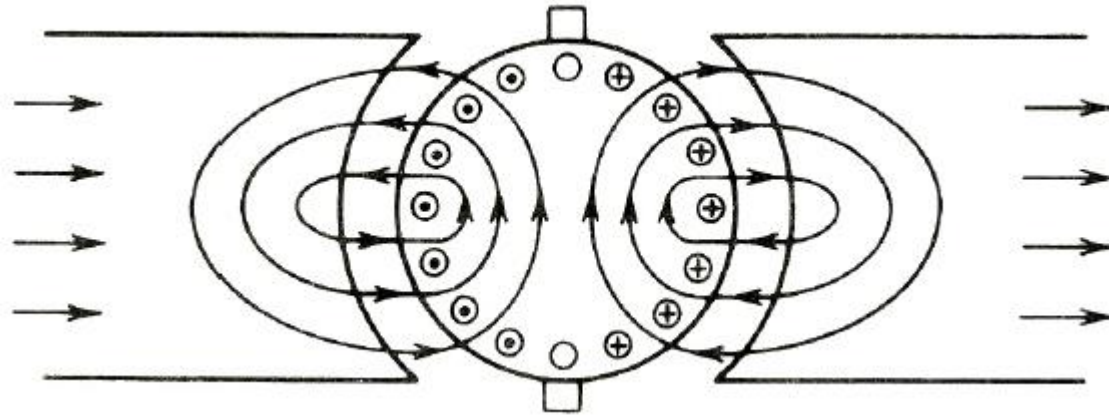


- ▶ When current flows in the armature circuit, it produces its own mmf
- ▶ The original flux distribution is reduced and known as *armature reaction*
- ▶ The net effect of armature reaction can be considered as reduction of field current

$$I_{f(eff)} = I_{f(actual)} - I_{f(AR)}$$




### 3.5 Armature Reaction

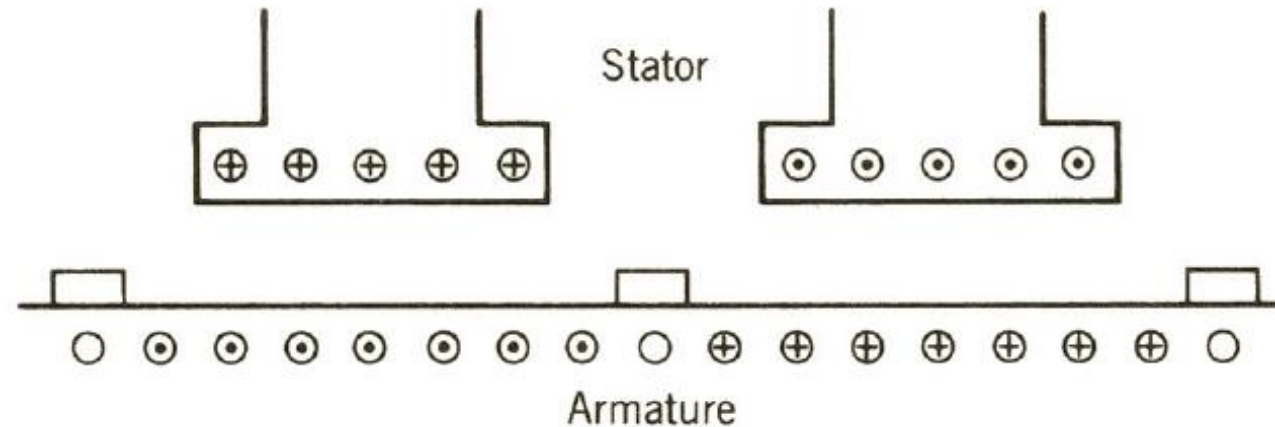

- The armature mmf distorts and demagnetizes the original flux density distribution
- It shifts zero flux density region and leads to sparking
- The armature reaction can be neutralized by a compensating winding

## Concept Check 3.2

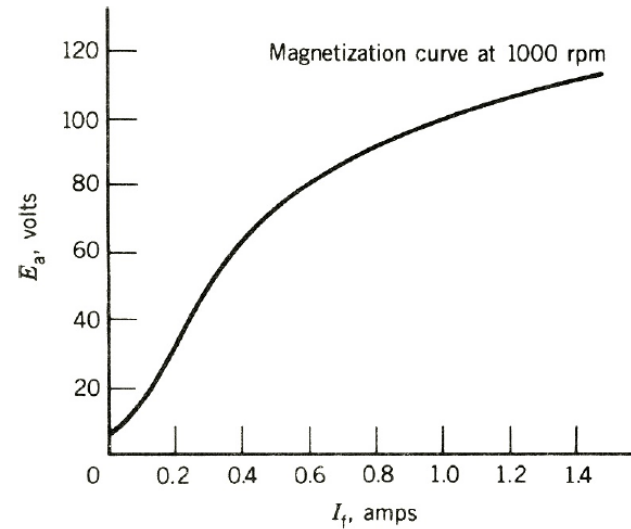

A 12 kW, 100 V, 1000 rpm dc shunt generator consists of armature resistance of  $0.1 \, \Omega$ , shunt field winding resistance of  $80 \, \Omega$  and field turns of 1200 turns per pole. The rated field current is 1 A. The magnetization characteristics at 1000 rpm is shown above. The machine is operated as a separately excited dc generator at 1000 rpm with rated field current.

- (a) Find the terminal voltage at full load (Ans: 88 V)
- (b) If the armature reaction is at full load of equivalent of 0.06 field amperes, find the full-load terminal voltage (Ans: 86 V)
- (c) Find the field current so as  $V_t = 100 \, \text{V}$  at full-load condition (Ans: 1.46 A)

# Concept Check 3.2

# Concept Check 3.2

## Concept Check 3.3

The DC machine in Concept Check 3.2 is now provided with series winding to become a compound DC machine. It is required to provide a terminal voltage of 100 V at no-load as well as full-load by cumulatively compounding the generator. Assume the series winding consists of resistance of  $0.01\ \Omega$ .

If the shunt field winding consists of 1200 turns per pole, how many series turns per pole are required to obtain zero voltage regulation, i.e., full load? (Ans: 5.04 turns per pole)

# Concept Check 3.3

# Concept Check 3.3

## Concept Check 3.4

The DC machine (12 kW, 100 V, 1000 rpm) in Concept Check 3.2 is connected to a 100 V DC supply and operated as a DC shunt motor. At no-load condition, the motor runs at 1000 rpm with armature of 6 A.

- (a) Find the value of resistance of the shunt field control rheostat (Ans: 21  $\Omega$ )
- (b) Find the rotation losses at 1000 rpm (Ans: 596.4 W)
- (c) Find the speed, electromagnetic torque and efficiency at rated condition if the air gap remains the same as that at no-load (Ans: 885.3 rpm; 113.9 Nm; 82.4 %)
- (d) Repeat (c) if the air gap flux is reduced by 5 % because of armature reaction (Ans: 931.9 rpm; 108.2 Nm; 82.4 %)
- (e) Find the stating torque if armature is limited to 150 % of its rated value (Ans: 170.8 Nm)
- (f) Repeated (e) if armature reaction is considered to be 0.16 A (Ans: 160.7 Nm)




# Concept Check 3.4

# Concept Check 3.4

# Concept Check 3.4

## 3.6 Speed Control

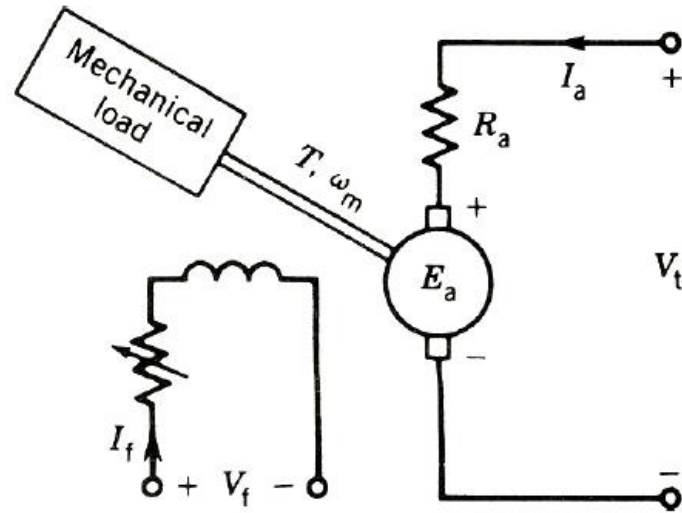


- ▶ DC motors are used to drive mechanical loads with speed controllability
- ▶ Consider a separately excited DC motor

$$E_a = K_a \Phi \omega_m = V_t - I_a R_a \qquad T = K_a \Phi I_a$$


$$\omega_m = \frac{V_t}{K_a \Phi} - \frac{R_a}{(K_a \Phi)^2} T$$

## 3.6 Speed Control

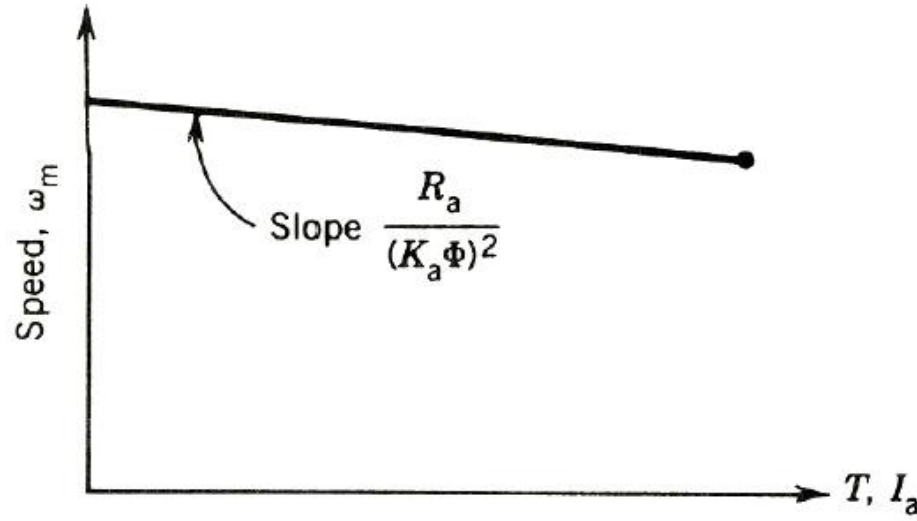



- The drop in speed as applied torque increases is small, and hence providing a good speed regulation
- Speed control can be achieved based on
  1. Armature voltage control
  2. Field control
  3. Armature resistance control

### 3.6.1 Armature Voltage Control

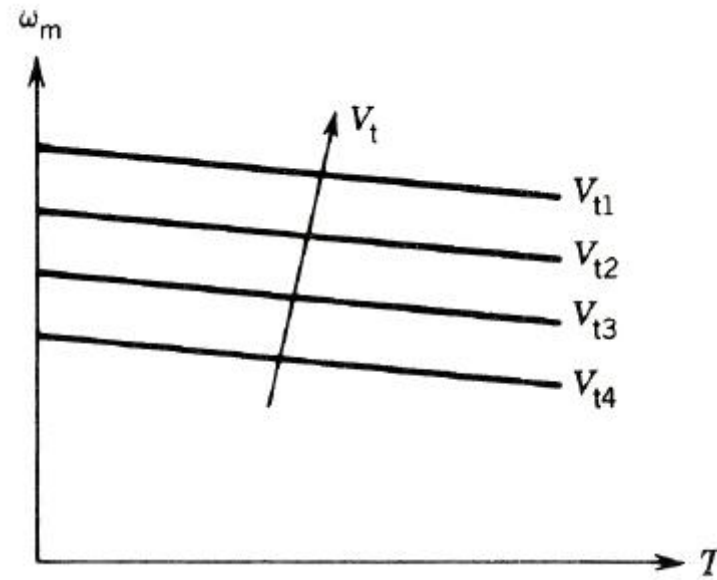


- Armature circuit resistance and field current are kept constant
- Armature terminal voltage is varied to change the speed linearly
- It provides smooth control from zero to base speed
- However, it is expensive because it needs a variable DC supply

### 3.6.1 Field Weakening

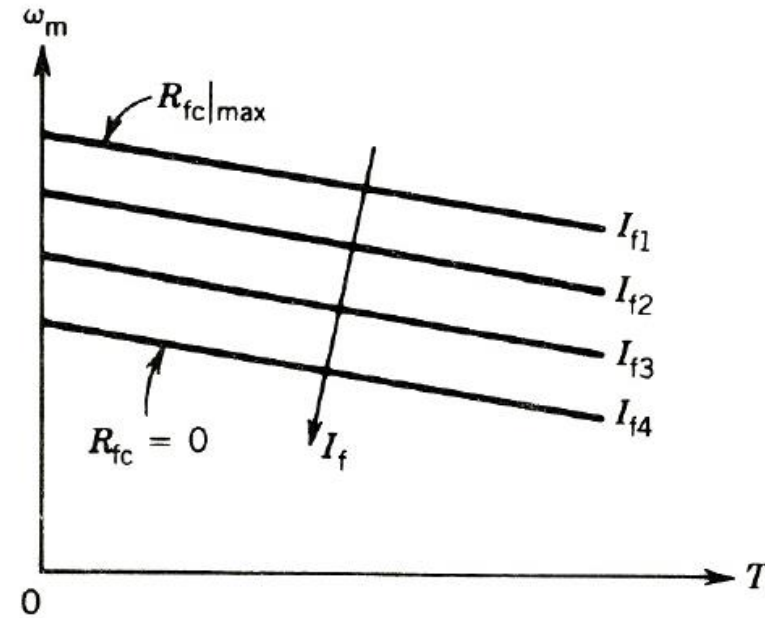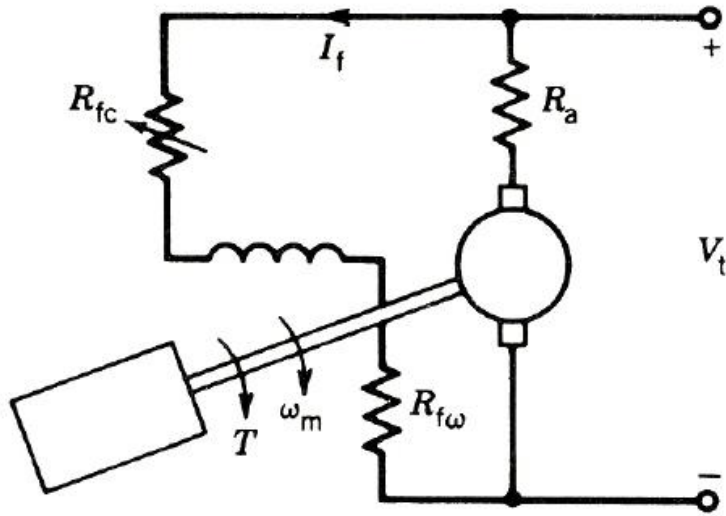

- Armature circuit resistance and terminal voltage are kept constant
- Field current is varied to change the speed linearly
- It can be achieved by using a field circuit rheostat
- Field current control is also known as *Field Weakening*



### 3.6.3 Combined Control

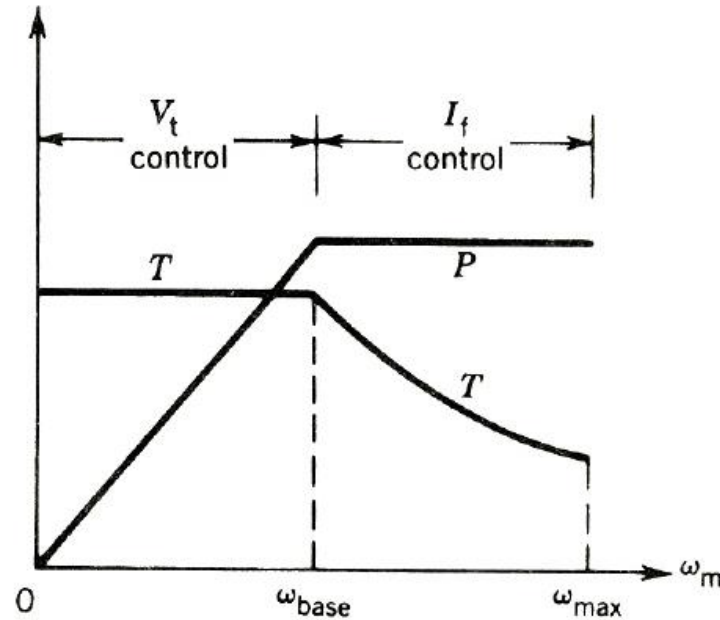

- Speed control from zero to base speed is obtained by armature voltage control, while this region is known as constant-torque region
- At the base speed, the armature terminal voltage is at rated value
- Speed control beyond the base speed is obtained by field weakening, while this region is known as constant-power region



### 3.6.4 Armature Resistance Control

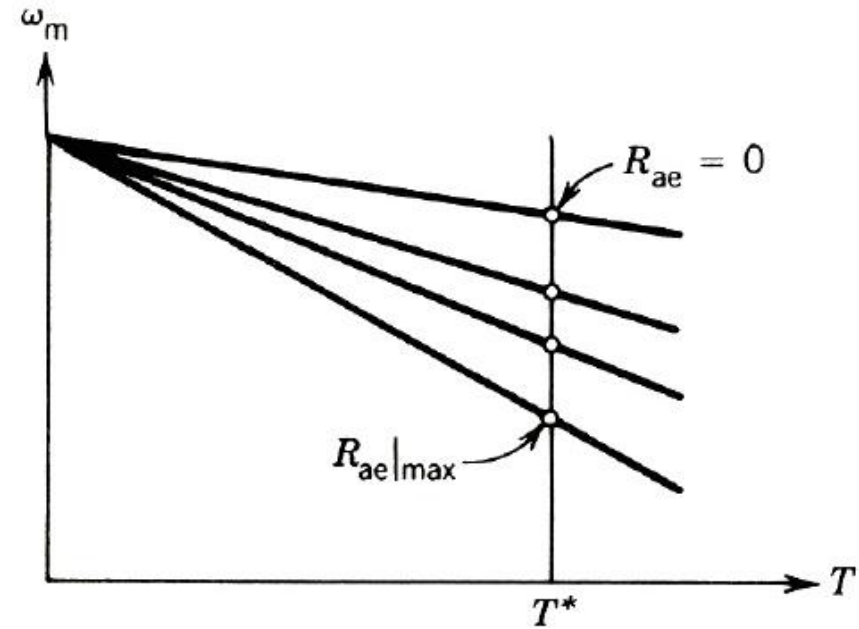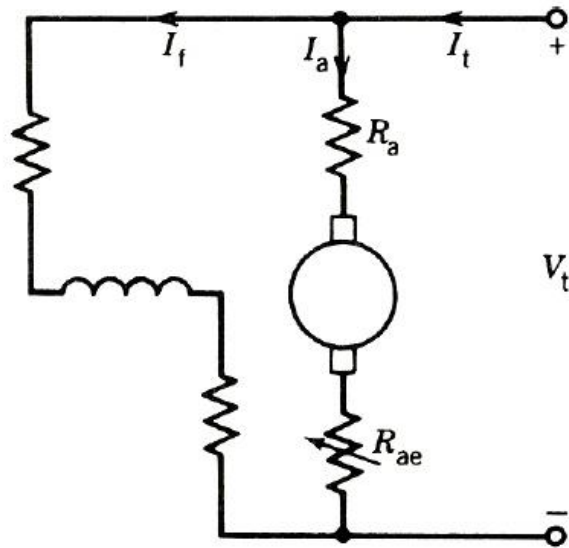

- ▶ Armature terminal voltage and field current are kept constant
- ▶ The speed is controlled by changing resistance in the armature circuit

$$\omega_m = \frac{V_t}{K_a \Phi} - \frac{R_a + R_{ae}}{(K_a \Phi)^2} T$$

- ▶ Less efficient than other two methods and more expensive than field control

## Concept Check 3.5



A variable-voltage source is supplied to a DC motor. By armature terminal voltage control from 0 to 500 V, the drive speed is varied from 0 to 1500 rpm, i.e., base speed.

- (a) Find the motor armature current if the torque is held constant at 300 Nm (Ans: 94.2 A)
- (b) Field weakening is applied when the speed is beyond its base speed while the armature voltage is held constant at 500 V. Find the torque available at a speed of 3000 rpm if the armature current is held constant at the value at (a) (Ans: 150 Nm)

# Concept Check 3.5

# Concept Check 3.5

### 3.6.5 Series Motor

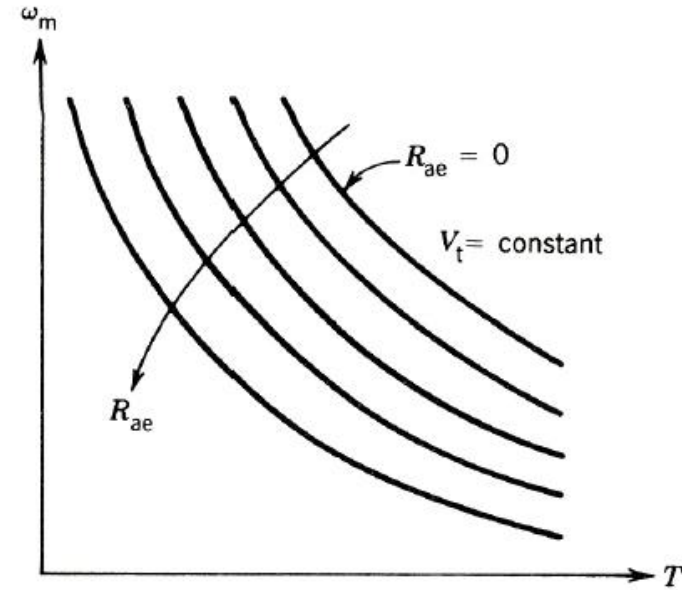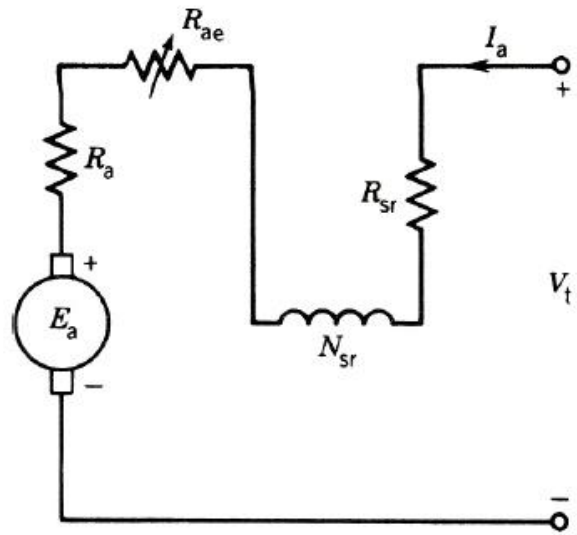


- ▶ An external resistance is connected in series to control the speed

$$\omega_m = \frac{V_t}{\sqrt{K_{sr}}\sqrt{T}} - \frac{R_a + R_{sr} + R_{ae}}{K_{sr}}$$

- ▶ A high torque is obtained at low speed and low torque at high speed

### 3.6.6 Types of Motor Controls

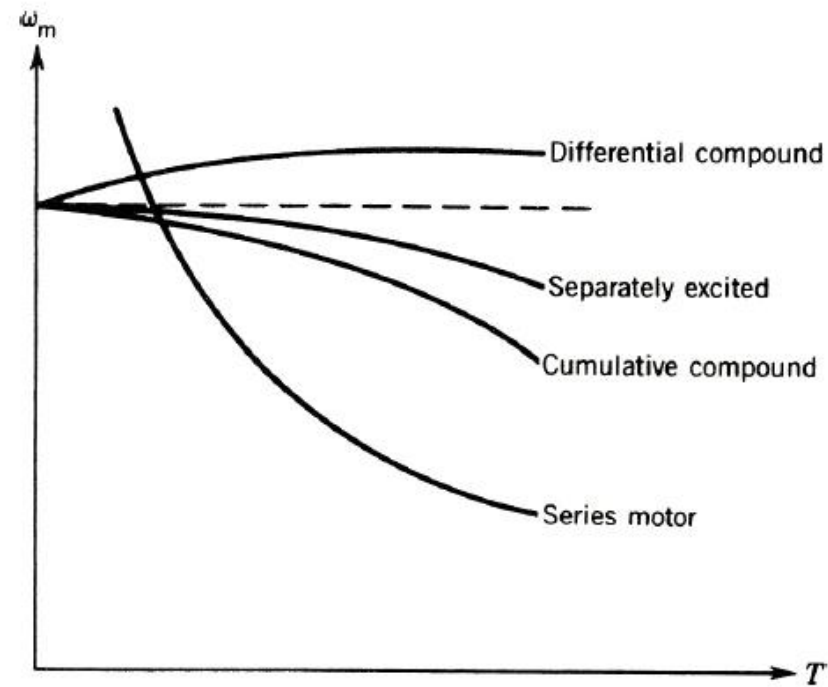

- Series can provide a variable speed characteristic over a very wide range

## Concept Check 3.6

A 220 V, 7 hp series motor is connected to a fan. It draws 25 A and spins at 300 rpm when it is connected to a 220 V supply with no external resistance. The required torque is proportional to the square of the speed. It consists of  $R_a = 6.0$  and  $R_{sr} = 0.4$  . Neglect armature reaction and rotational loss.


- (a) Find the power delivered to the fan and the torque developed by the machine (Ans: 6.54 hp; 155.2 Nm)
- (b) If the speed is reduced to 200 rpm by adding a resistance in armature circuit, find the value of this resistance and the power delivered by the fan (Ans: 69.0 Nm; 1.94 hp)

# Concept Check 3.6



# Concept Check 3.6

## 3.7 Starting Resistance

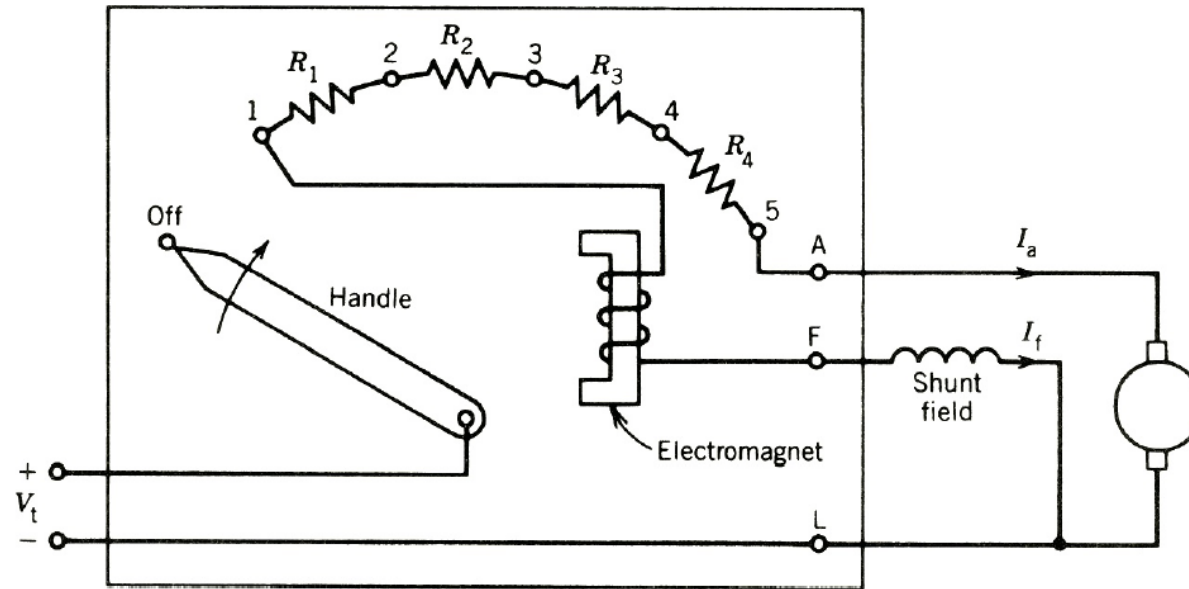

- If DC motor is connected to a DC source directly, the starting current will be too large
- An external resistance is purposely added when starting a DC motor
- Since back EMF increases as speed, the external resistance can be gradually taken off

## Concept Check 3.7

A 10 kW, 100 V, 1000 rpm DC machine has  $R_a = 0.1 \, \Omega$  and connected to a 100 DC source

- (a) Find the starting current if no starting resistance is used (Ans: 1000 A)
- (b) Find the value of the starting resistance if the starting current is limited to twice of the rated current (Ans:  $0.4 \, \Omega$ )
- (c) By using a starter box, the DC machine is to be operated as a motor. Find the values of required resistances such that the armature current is kept to be within 100 to 200 % of the rated value during starting up (Ans:  $0.25 \, \Omega$ ;  $0.125 \, \Omega$ ;  $0.025 \, \Omega$ )

# Concept Check 3.7

# Concept Check 3.7