

### **Problem Set 4 Power Converters**

1. A 110 V, 5 hp DC motor is controlled by a single-phase AC/DC full converter. The motor voltage constant is 0.055 V/rpm. The AC supply is 120 V, 60 Hz. Assume the DC motor and converter are ideal and a very large inductance is connected in series with the motor. For a speed of 1000 rpm and rated motor current, find
  - a. The firing angle of the converter.
  - b. The rms value of the supply current
  - c. The rms value of thyristor current.
  
2. A three-phase full converter is used to control the speed of a DC motor. The motor consists of voltage constant of 0.1 V/rpm and armature resistance of 0.2  $\Omega$ . The supply line-to-line voltage is 110 V. For firing angle of 50°, the motor speed is 900 rpm.
  - a. Assume the motor current is ripple-free, find the average value of the motor current.
  - b. Find the thyristor current.
  - c. Find the supply line current.
  
3. A single-phase AC/DC full converter is used to control a DC motor with resistance of 0.25  $\Omega$ , motor constant of 0.1 V/rpm and very large inductance. The AC supply is 120 V, 60 Hz. At firing angle of 60°, the motor current is continuous with average value of 20 A and ripple of 20 %. Find
  - a. The speed of the motor.
  - b. The power loss in armature resistance.
  - c. The power developed by the motor.
  
4. A one-quadrant step-down converter with switching frequency of 250 Hz is used to control the speed of a DC motor with resistance of 0.15  $\Omega$  and motor constant of 0.05 V/rpm. The supply DC voltage is 120 V. At a speed of 1200 rpm, the motor draws current of 125 A. Assume the motor current is ripple-free.
  - a. Find the duty ratio of the converter and its on-time.
  - b. Draw waveform of output voltage, output current and supply current.
  - c. Find the developed torque by the armature.
  - d. Find the power taken by the motor.
  - e. Find the power drawn from the supply.

### Answer

1.

(a)

$$V_o = 0.055 \times 1000 = 55V$$

$$I_o = \frac{5 \times 746}{110} = 33.9A$$

$$V_o = \frac{2\sqrt{2} \cdot V}{\pi} \cos \alpha = 108.02 \cos \alpha = 55V$$

$$\alpha = 60^\circ$$

(b)

$$I = I_o = 33.9A$$

(c)

$$I_{Th} = \frac{33.9}{\sqrt{2}} = 23.97A$$

2.

(a)

$$V_o = \frac{3\sqrt{2} \times 110}{\pi} \cos 50^\circ = 95.4729V$$

$$E_a = 0.1 \times 900 = 90V$$

$$I_o = \frac{95.4729 - 90}{0.2} = \frac{5.4729}{0.2} = 27.3643A$$

(b)

$$I_{Th} = \frac{27.3643}{\sqrt{3}} = 15.8A$$

(c)

$$I_{Lim} = \sqrt{\frac{2}{3}} \times 27.3643 = 22.3429A$$

3.

(a)

$$V_o = \frac{2 \times \sqrt{2} \times 120}{\pi} \cos 60^\circ = 54V$$

$$E_a = 54 - 0.25 \times 20 = 49V$$

$$n = \frac{49}{0.1} = 490rpm$$

(b)

$$I_o = 20A, I_o(rms) = \sqrt{20^2 + (0.2 \times 20)^2} = 20.4A$$

where  $(0.2 \times 20)^2$  is ripple content

$$P_R = 20.4^2 \times 0.25 = 105W$$

(c)

$$P_a = E_a I_o = 49 \times 20 = 980W$$

4.

(a)


$$V_o = E_a + I_a R_a = 0.05 \times 1200 + 125 \times 0.15 = 78.75V$$

$$T = \frac{10^3}{250} msec = 4msec$$

$$\alpha = \frac{78.75}{120} = 0.6563$$

$$t_{on} = \alpha T = 0.6563 \times 4 = 2.625msec$$

(b)

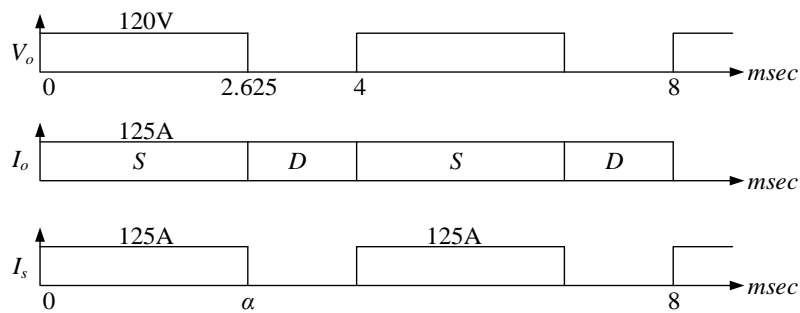

(c)

$$E_a T_o = 60 \times 125 = 7500W$$

$$T = \frac{7500}{1200 / 60 \times 2\pi} = 59.683N \cdot m$$

(d)

$$P_o = V_o I_o = 78.75 \times 125 = 9844W$$

(e)

$$P_s = 120 \times 82.03 = 9844W$$