

Problem Set 4 Power Converters

1. A 110 V, 5 hp DC motor is controlled by a single-phase AC/DC full converter. The motor voltage constant is 0.055 V/rpm. The AC supply is 120 V, 60 Hz. Assume the DC motor and converter are ideal and a very large inductance is connected in series with the motor. For a speed of 1000 rpm and rated motor current, find
 - a. The firing angle of the converter.
 - b. The rms value of the supply current
 - c. The rms value of thyristor current.

2. A three-phase full converter is used to control the speed of a DC motor. The motor consists of voltage constant of 0.1 V/rpm and armature resistance of 0.2 Ω . The supply line-to-line voltage is 110 V. For firing angle of 50°, the motor speed is 900 rpm.
 - a. Assume the motor current is ripple-free, find the average value of the motor current.
 - b. Find the thyristor current.
 - c. Find the supply line current.

3. A single-phase AC/DC full converter is used to control a DC motor with resistance of 0.25 Ω , motor constant of 0.1 V/rpm and very large inductance. The AC supply is 120 V, 60 Hz. At firing angle of 60°, the motor current is continuous with average value of 20 A and ripple of 20 %. Find
 - a. The speed of the motor.
 - b. The power loss in armature resistance.
 - c. The power developed by the motor.

4. A one-quadrant step-down converter with switching frequency of 250 Hz is used to control the speed of a DC motor with resistance of 0.15 Ω and motor constant of 0.05 V/rpm. The supply DC voltage is 120 V. At a speed of 1200 rpm, the motor draws current of 125 A. Assume the motor current is ripple-free.
 - a. Find the duty ratio of the converter and its on-time.
 - b. Draw waveform of output voltage, output current and supply current.
 - c. Find the developed torque by the armature.
 - d. Find the power taken by the motor.
 - e. Find the power drawn from the supply.

Answer

- | | | | |
|----------------------|-------------|------------|------------|
| 1. (a) 60° | (b) 33.9 A | (c) 24.0 A | |
| 2. (a) 27.4A | (b) 15.8 A | (c) 22.3 A | |
| 3. (a) 490 rpm | (b) 105 W | (c) 980 W | |
| 4. (a) 0.66; 2.64 ms | (c) 59.7 Nm | (d) 9844 W | (e) 9844 W |